

Combinational Circuits: Multiplexers, Decoders, Programmable Logic Devices

Lecture 5
Doru Todinca

Textbook

- This chapter is based on the book [RothKinney]: Charles H. Roth, Larry L. Kinney, *Fundamentals of Logic Design*, Sixth Edition, Cengage Learning. 2010
- Figures, tables and text are taken from this book, Unit 9, **Multiplexers, Decoders, and Programmable Logic Devices**, if not stated otherwise
- Figure numbers are those from [RothKinney]

Multiplexers

- A multiplexer (MUX) is a circuit that has
 - Data inputs
 - Control inputs
 - An output
- The control inputs select which data inputs to be connected to the output
- Figure 9.1 ([RothKinney]) show a 2:1 MUX and its model as a switch

Multiplexers

FIGURE 9-1
2-to-1 Multiplexer
and Switch Analog

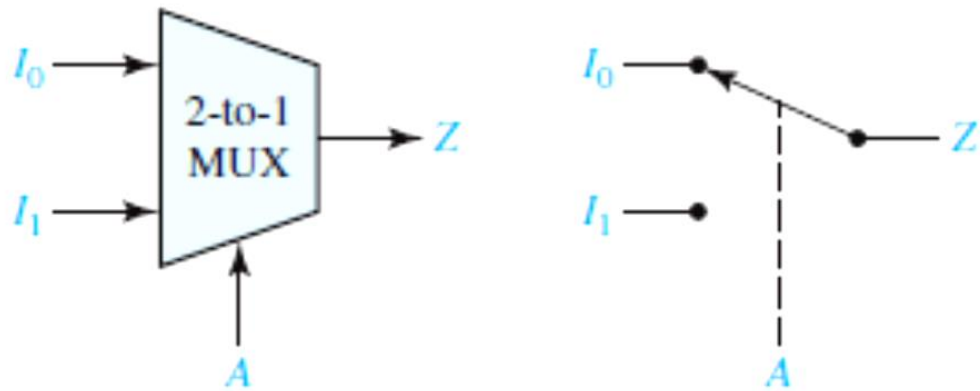


Figure 9-1 A 2:1 MUX and switching analog [RothKinney]

Multiplexers


- When the control input A is 0, data input I_0 will be connected to the output Z (i.e. $Z=I_0$)
- When $A=1$ we will have $Z=I_1$.
- The logic equation for the 2:1 MUX is:

$$Z = A' \cdot I_0 + A \cdot I_1$$

- Figure 9.2 shows 4:1, 8:1 and $2^n:1$ multiplexers and their corresponding logic functions
 - here 4, 8, 2^n is the number of data inputs
- Of course, the number of control inputs for a $2^n:1$ MUX must be n .



Multiplexers

FIGURE 9-2
Multiplexers

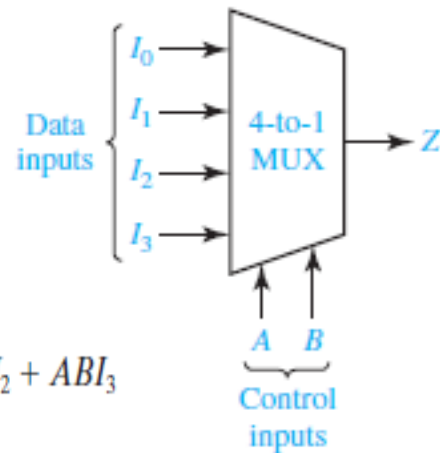

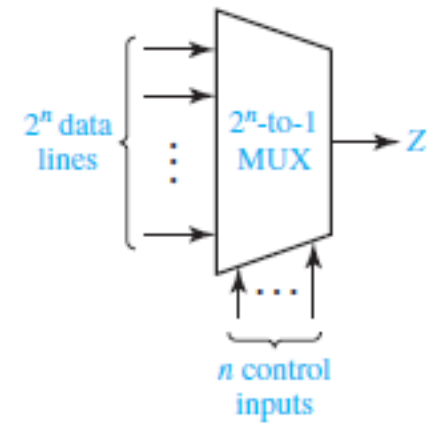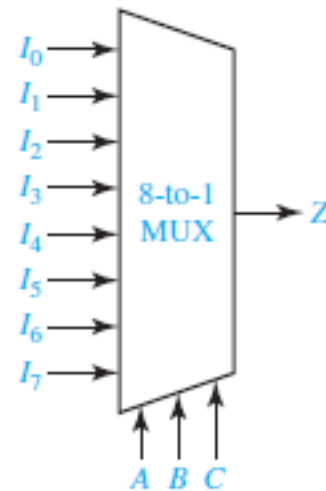4:1 mux:

$$Z = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$$



$$2^n:1 \text{ MUX: } Z = \sum_{k=0}^{2^n-1} m_k I_k$$

$$\begin{aligned} 8:1 \text{ MUX: } Z = & A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3 \\ & + AB'C'I_4 + AB'CI_5 + ABC'I_6 + ABCI_7 \end{aligned}$$

Figure 9-2: Multiplexers: 4:1 mux, 8:1 mux, 2^n :1 mux [RothKinney]

Logic diagram for the 8:1 MUX

FIGURE 9-3
Logic Diagram for
8-to-1 MUX

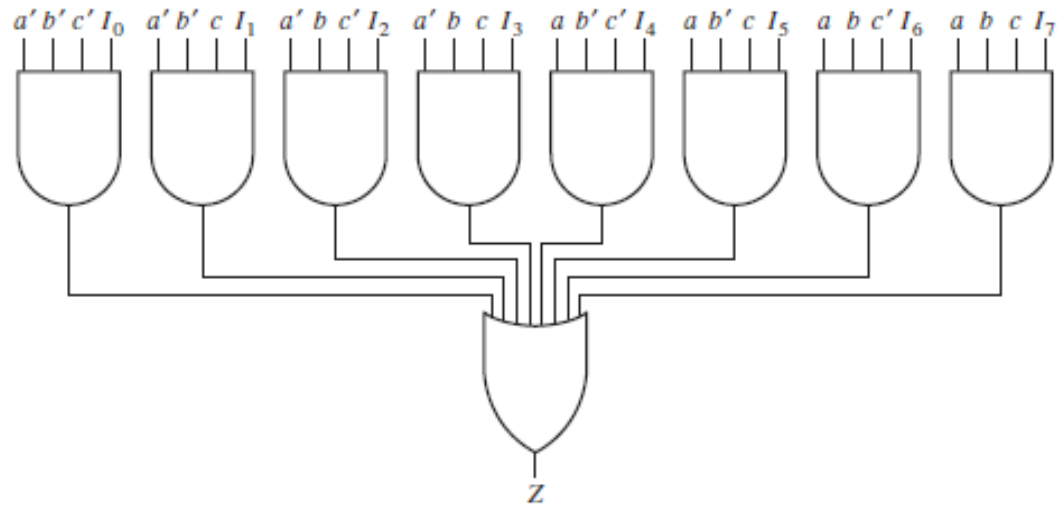


Figure 9-3. Logic diagram for for 8:1 MUX [RothKinney]

Example of MUX application

- Multiplexers are frequently used to select between two vectors (words) of data, like in figure 9.4
- If $A=0$, the 4-bit vector z will take the values x :
 - $x_3 x_2 x_1 x_0$ will be connected to $z_3 z_2 z_1 z_0$
- If $A=1$, the vector z will take the values y :
 - y_3 will connect to z_3 , ..., y_0 will connect to z_0 .

FIGURE 9-4
Quad Multiplexer
Used to Select Data

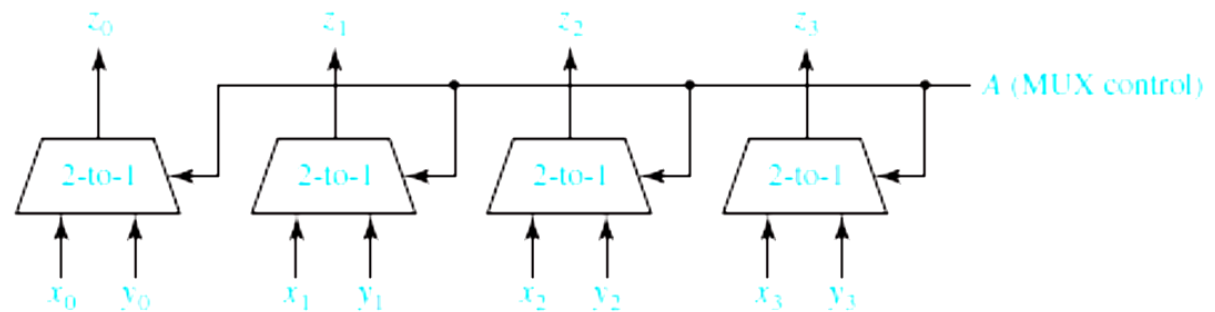


Fig 9-4. Four bit signals multiplexed together [RothKinney]

FIGURE 9-5
Quad Multiplexer
with Bus Inputs and
Output

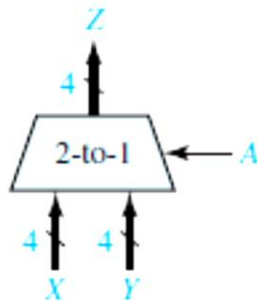


Fig 9-5. The equivalent representation with buses of fig 9-4 [RothKinney].

Buses

- Several logic signals that perform a common function may be grouped together to form a *bus*.
- We represent a bus by a single, heavy line, with the number of lines specified near the bus line using a slash
- Figure 9.4 can be equivalently represented in figure 9.5 using 4-bit buses
- Instead of using small letters for x , y and z , we use capital letters for buses: X , Y , Z .
- X bus consists on signals x_3 , x_2 , x_1 and x_0 , and similar for Y and Z .

Enable inputs

- The multiplexers can have the outputs active high (like in previous figures), or active low.
- If a signal is active low, we use an inverting bubble on the circuit diagram, for that signal
- A multiplexer, like many other circuits, can have additional *enable* inputs:
 - When the enable input is active, the circuit (mux in this case) works normally
 - When the enable input has the inactive value, the circuit's outputs are all inactive: all 0 if they are active high, all 1 if they are all active low, or all in high-impedance (see later tri-state buffers).

Buffers

- The number of circuit inputs that can be driven by a single output is limited
- If a circuit output must drive many inputs, we use *buffers* to increase the driving capability
- In figure 9.6 the buffer (having the output F) is a noninverting buffer: it does not perform any logic function, i.e. its logic equation is $F=C$.
- It only increases the driving capability

Non-inverting buffer

FIGURE 9-6
Gate Circuit with
Added Buffer

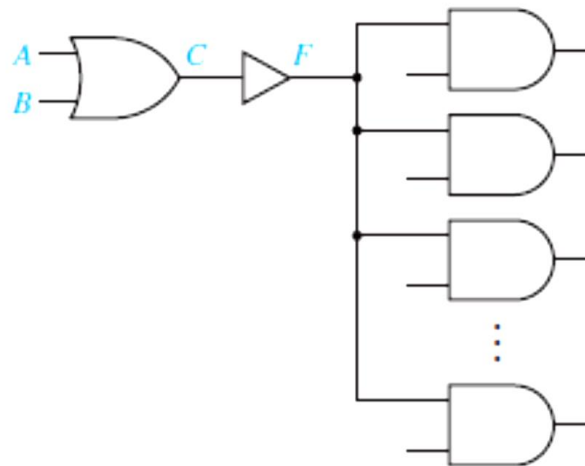


Fig 9-6. Circuit with added buffers [RothKinney]

Three-state buffers

- Normally the outputs of two circuits cannot be connected together
- If they were connected, and if one output is 0 and the other output is 1
 - the resulted voltage can be between LOW (logic 0) and HIGH (logic 1)
 - Hence, an undecided logic value
 - Or even the circuits can be damaged
- Sometimes it is necessary to connect two outputs, under the condition that they will not be simultaneously active
- The de-activation of an output can be realized using three-state buffers
- Figure 9.7 shows a three-state buffer and its logical equivalent

Three-state buffers

- Normally, there is a path between the output of a circuit and
 - either GND (ground) $\Rightarrow V_{\text{out}}=\text{LOW}$, or V_{CC} (+5V) $\Rightarrow V_{\text{out}}=\text{HIGH}$
- There are circuits (buffers) for which the paths to GND and V_{CC} are both blocked
- The output of the buffer is then in a high-impedance state, called Hi-Z (the third state)
- No current can flow in the buffer's output, the buffer has a very high resistance (impedance)
- Logically, it is as if the output of the buffer is disconnected (see figure 9.7)
- Three-state buffers are called also tri-state buffers
- The three state buffers have an enable input (B in figure 9.8) that determines if the buffer functions as a normal buffer, or its output is in Hi-Z
- The command and the output can be inverting or non-inverting

Tri-state buffers

Fig 9-7. Tri-state buffer [RothKinney]

FIGURE 9-7
Three-State Buffer


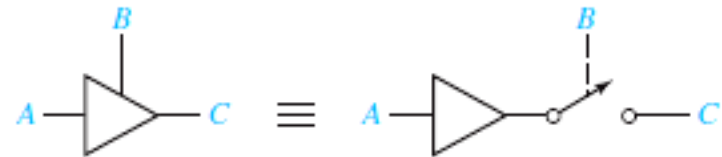


Fig 8. Kinds of tri-state buffers [RothKinney]

FIGURE 9-8
Four Kinds of
Three-State Buffers

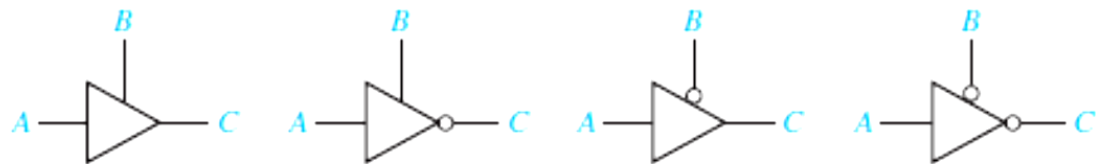

B	A	C
0	0	Z
0	1	Z
1	0	0
1	1	1

(a)

B	A	C
0	0	Z
0	1	Z
1	0	1
1	1	0

(b)

B	A	C
0	0	0
0	1	1
1	0	Z
1	1	Z

(c)

B	A	C
0	0	1
0	1	0
1	0	Z
1	1	Z

(d)

Tri-state buffers and logic values

- In figure 9.9, the outputs of two buffers are connected together, but only one of the two outputs is active at a time, the other is in Hi-Z
- The circuit is logically equivalent to a 2:1 multiplexer
- For the circuit from figure 9.10, if both buffers are enabled and if $A=0$ and $C=1$, then the value of the output F will be unknown.
- We denote by X the unknown logical value
- A bus driven by tri-state buffers is called a tri-state bus
- The signals on the bus can have the values 0, 1, Z and maybe X .
- Table 1 presents the resulting value of two signals $S1$ and $S2$ connected together and having these logic values

Tri-state buffers for data selection

FIGURE 9-9
Data Selection
Using Three-State
Buffers

 


Fig 9-9. Data selection using three state buffers and the logically equivalent circuit [RothKinney]

Logic values for buses signals

FIGURE 9-10
Circuit with Two
Three-State Buffers

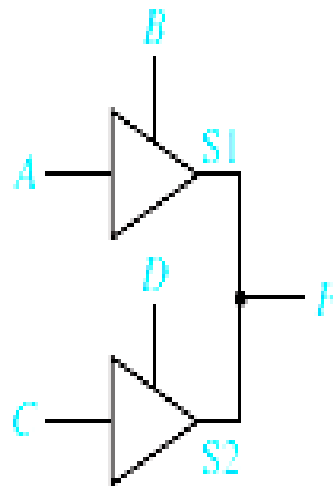


Fig 9-10. Circuit with tri-state buffers [RothKinney]

		S2			
		X	0	1	Z
S1	X	X	X	X	X
	0	X	0	X	0
	1	X	X	1	1
	Z	X	0	1	Z

Table 1: Logic values for bus signals and the resulting value when they are connected together [RothKinney]

Interpretation of table 1

- Normally we do not connect several circuit outputs together
- If there are situations when we have to, we use tri-state buffers and an arbitration mechanism that ensures that only one output has a logic value, and the other outputs are in Hi-Z
- If the arbitration mechanism fails, two active (i.e, not in Hi-Z) circuits outputs can be connected together
- If they have different logic values (0 and 1), the resulted value is unknown, denoted X
 - in the table 0 and 1 give X
- Such an unknown value propagates, in the sense that, if a third circuit output is also connected, the resulting value will remain X
 - In table 1, X and any value give X
- From the table it seems ok to connect together two circuit outputs that are both 0 or both 1
- In reality it is not ok, mainly due to transition periods (when circuits change value)
- When no output is active, the resulted value will be Hi-Z

Table 1 and VHDL

- In VHDL we cannot connect two circuit outputs together
 - a signal cannot have more than one source (driver)
- If we need a signal with more than one driver, it is declared in a special way and it has a *resolution function*, that determines the resulted value of the signal
- A resolution function works like described in table 1:
 - An X results from a 0 and a 1
 - X is stronger than any other value
 - 0 and 1 are stronger than Z
 - The final result will be Z only if all values are Z

Bi-directional pins

- Circuit from figure 9.11 shows an example of using tri-state buffers as a means to select one of several (4 in this case) sources
- The circuit behaves like a 4:1 MUX
- Figure 9.12 shows another utilization of tri-state buffers, for circuits with bi-directional pins
 - A pin is used both for input and output, but not in the same time
 - Such situation appears e.g. for data buses at microprocessors
 - Multiplexing reduces the number of pins, which reduces the cost of the circuit

Applications of tri-state circuits

Fig 9-11. Four sources for one operand
[RothKinney]

FIGURE 9-11
4-Bit Adder with
Four Sources for
One Operand

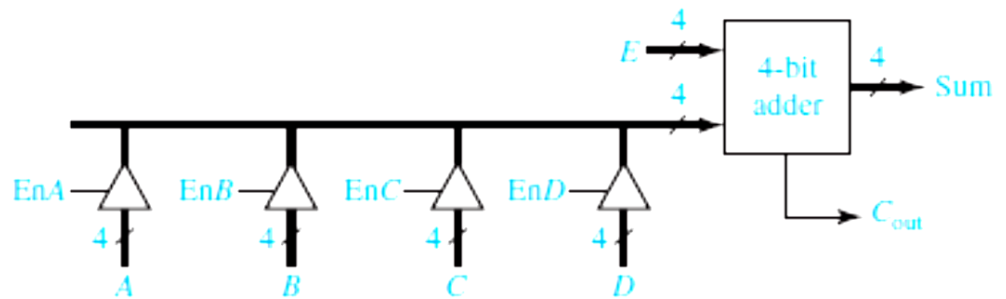


Fig 9-12. Circuit with
bi-directional input-
output pins
[RothKinney]

FIGURE 9-12
Integrated Circuit
with Bi-Directional
Input-Output Pin


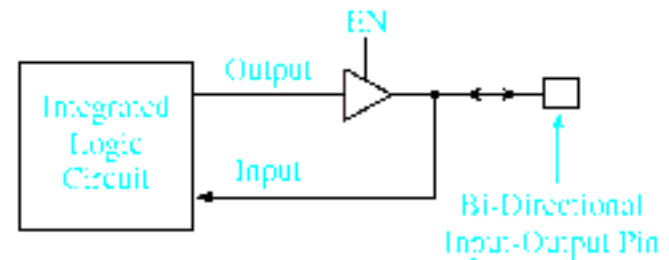


Fig 6-54
[Wakerly]: The
74x541 octal
tristate buffer:
(a) logical
diagram; (b)
logical symbol

The circuit is
used in
microprocessor
systems for
connecting
peripheral
devices (they
have 8 data
bits)


Inputs G1_L
and G2_L:
enable inputs.

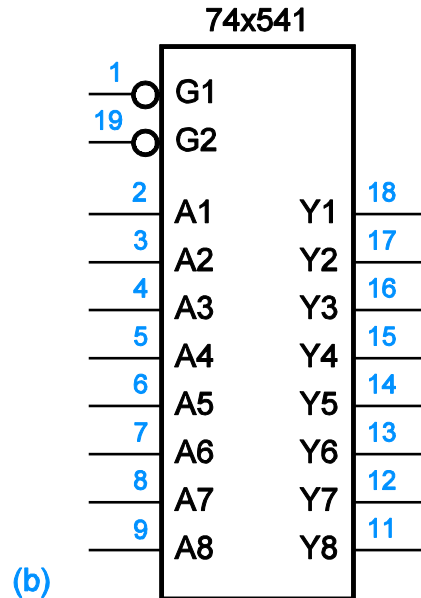
Symbol on gates means
hysteresis: improved noise
immunity



Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

(a)

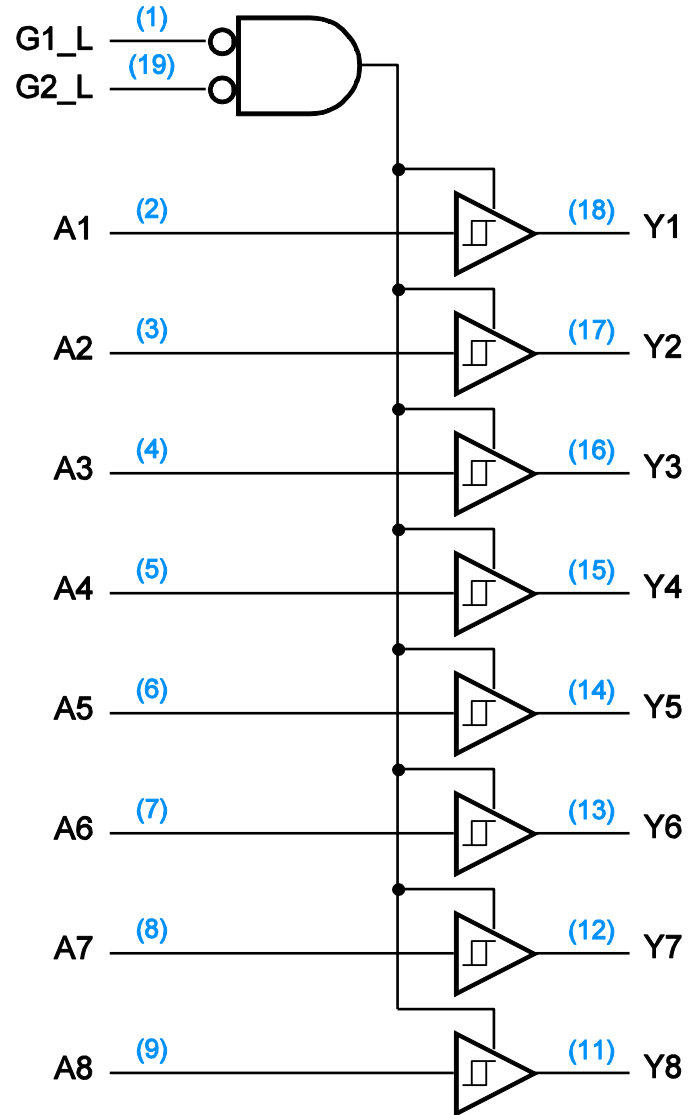

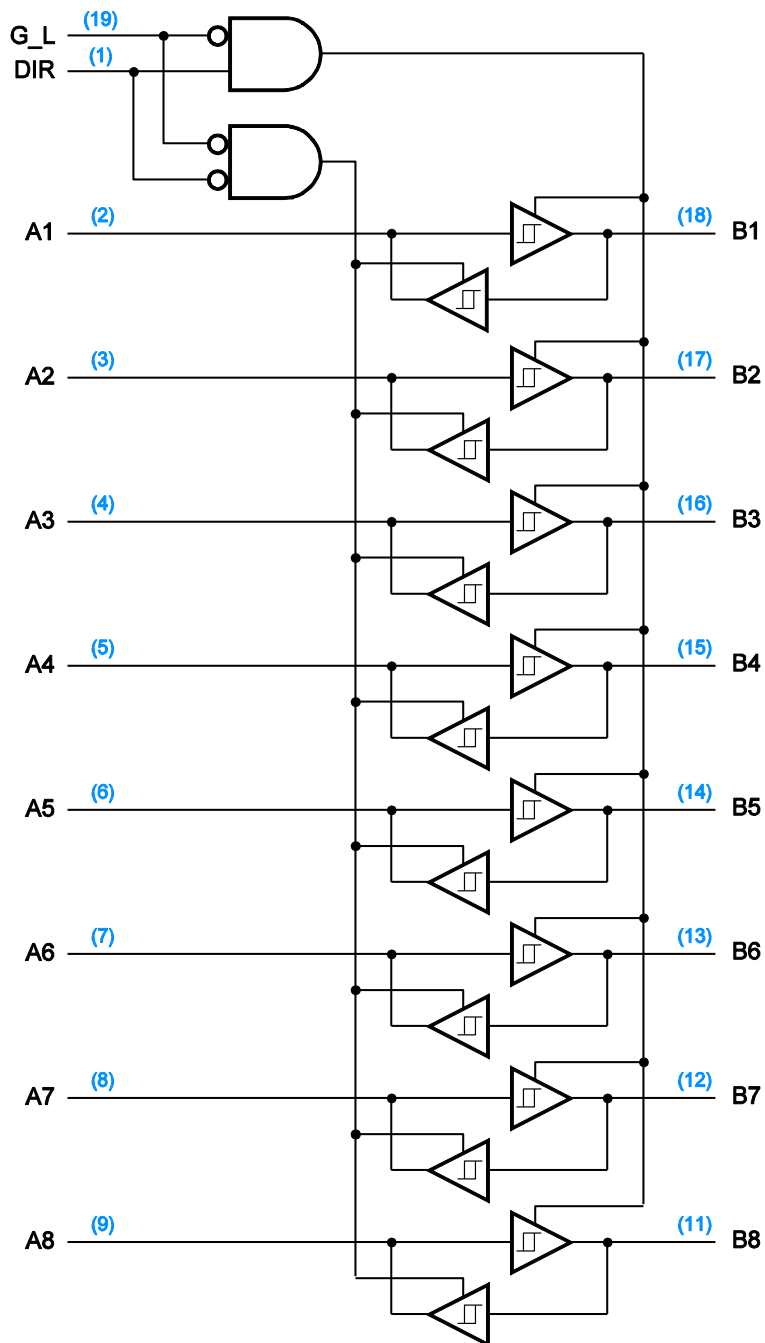

(a)

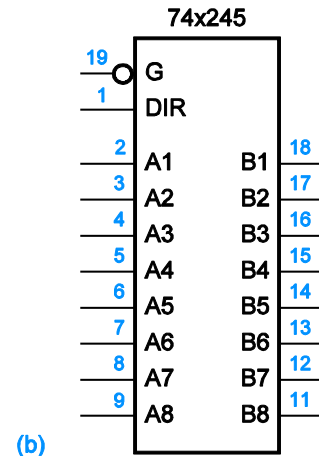


Fig 6-56
[Wakerly]
74x245 octal
tri-state
transceiver: (a)
logic diagram;
(b) logic symbol

Bus transceiver: contains pairs of tri-state buffers connected in opposite directions: from A to B if DIR=1, or from B to A if DIR=0

Buffers are enabled only if G_L=0

The circuit is used typically between two busses.

Decoders and Encoders

- Figure 9.13 shows a 3-to-8 decoder
 - The inputs represent a 3-bits binary number (between 0 and 7)
 - The active output corresponds to the decimal representation of the input number (e.g, if input is 101, output 5 will be active)
- Exactly one output will be active for each input combination
- The decoder generates all the minterms for three input variables
- In general a n -to- 2^n decoder generates all minterms for n variables
- The outputs are given by the equations $y_i = m_i$ (for non-inverting outputs) and $y_i = m_i' = M_i$ for inverting outputs
- Figure 9.14 shows a 4-to-10 decoder with inverted outputs: logic diagram, block diagram and truth table
- The 4-to-10 decoders do not generate all possible minterms

3-to 8 Decoder

FIGURE 9-13
A 3-to-8 Line
Decoder



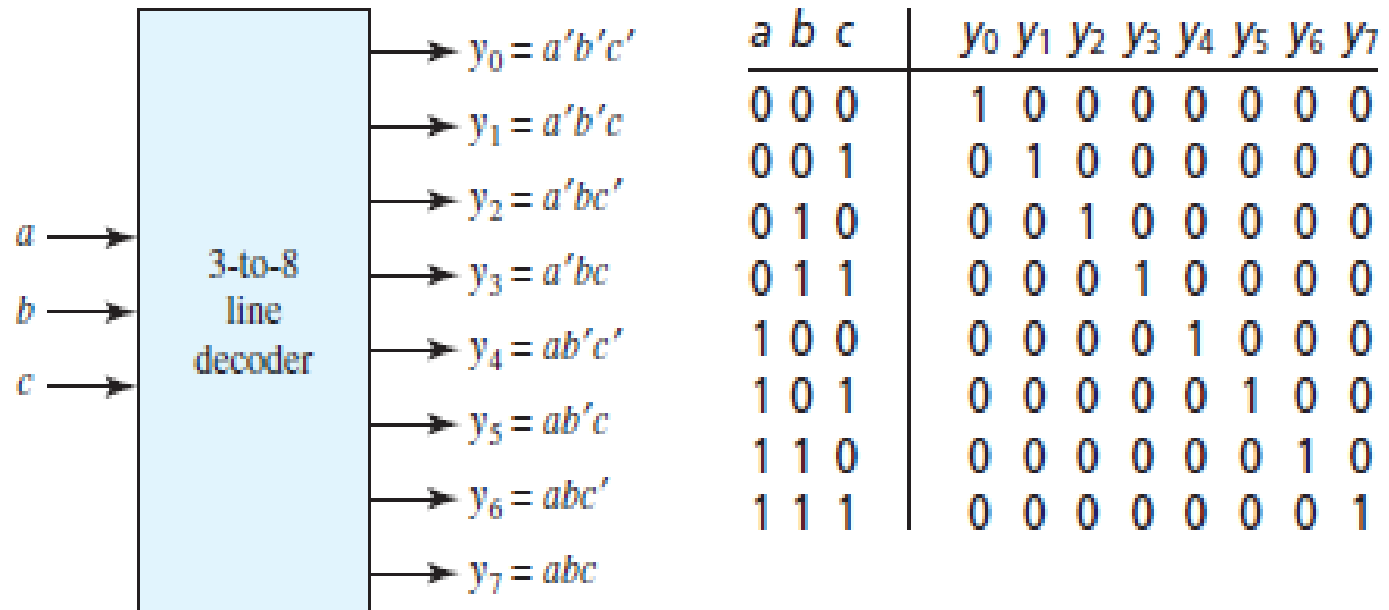


Figure 13. A 3-to-8 decoder [RothKinney]

4-to-10 decoder

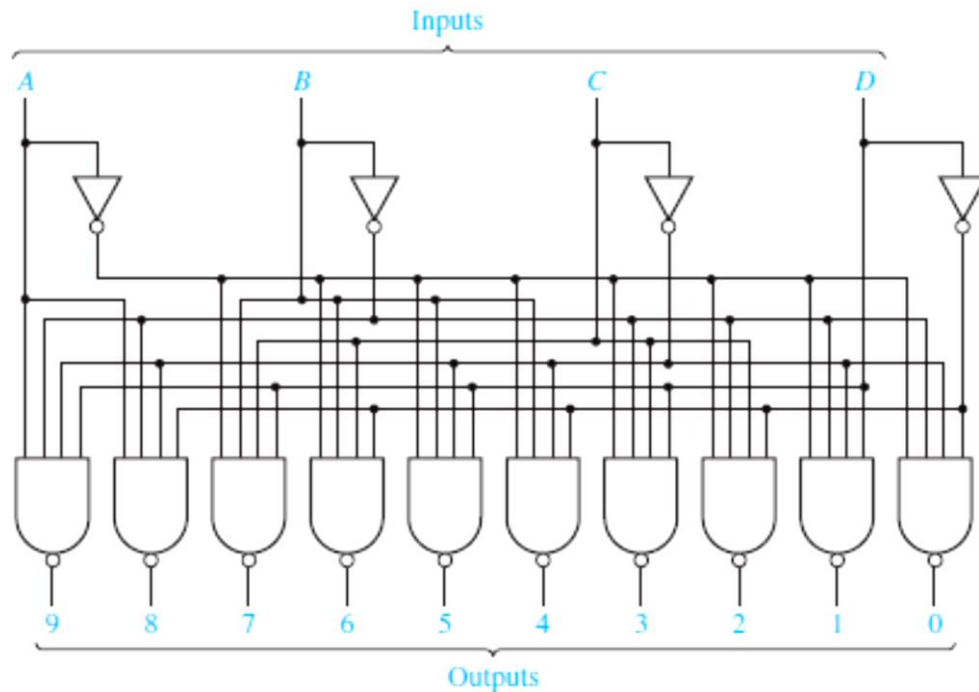

(a) Logic diagram

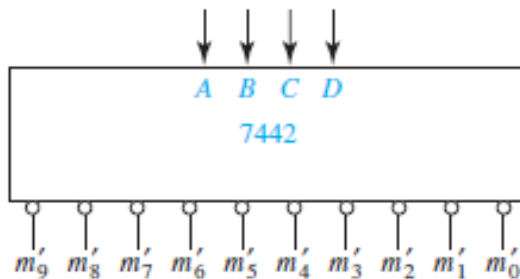

(b) Block diagram

BCD Input				Decimal Output									
A	B	C	D	0	1	2	3	4	5	6	7	8	9
0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	0	0	1	1	0	1	1	1	1	1	1	1	1
0	0	1	0	1	1	0	1	1	1	1	1	1	1
0	0	1	1	1	1	0	1	1	1	1	1	1	1
0	1	0	0	1	1	1	1	0	1	1	1	1	1
0	1	0	1	1	1	1	1	0	1	1	1	1	1
0	1	1	0	1	1	1	1	1	0	1	1	1	1
0	1	1	1	1	1	1	1	1	1	0	1	1	1
1	0	0	0	1	1	1	1	1	1	1	0	1	1
1	0	0	1	1	1	1	1	1	1	1	1	0	1
1	0	1	0	1	1	1	1	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1	1	1	1	1	1
1	1	0	0	1	1	1	1	1	1	1	1	1	1
1	1	0	1	1	1	1	1	1	1	1	1	1	1
1	1	1	0	1	1	1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1	1	1	1	1	1	1

(c) Truth Table

FIGURE 9-14
A 4-to-10 Line Decoder

Fig 9-14. A 4-to10 decoder [RothKinney]

Generic 2-to-4 decoder with enable

Table 5-4

Truth table for a 2-to-4
binary decoder.

<i>Inputs</i>			<i>Outputs</i>			
EN	I1	I0	Y3	Y2	Y1	Y0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Truth table for a 2-to-4 binary decoder
[Wakerly]

Generic 2-to-4 decoder with enable

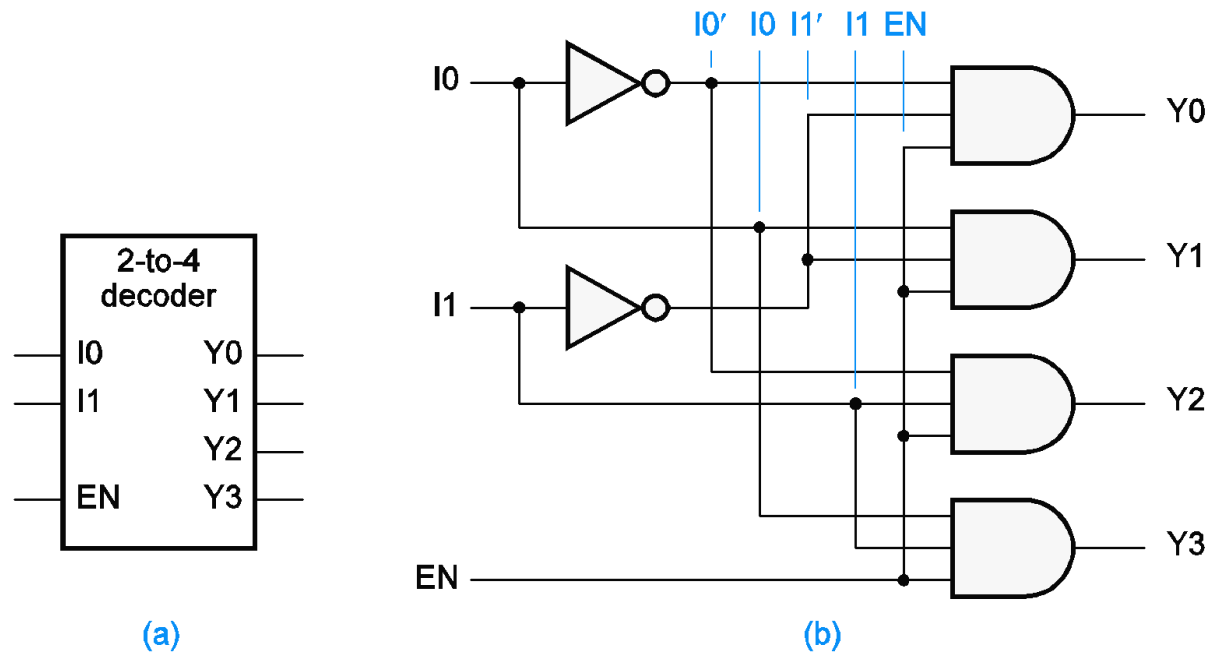



Fig 6.32. A 2-to-4 decoder: (a) inputs and outputs; (b) logic diagram [Wakerly]

Commercial 2-to-4 decoder



Table 5-6
Truth table for one-
half of a 74x139 dual
2-to-4 decoder.

<i>Inputs</i>			<i>Outputs</i>			
G_L	B	A	Y3_L	Y2_L	Y1_L	Y0_L
1	x	x	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

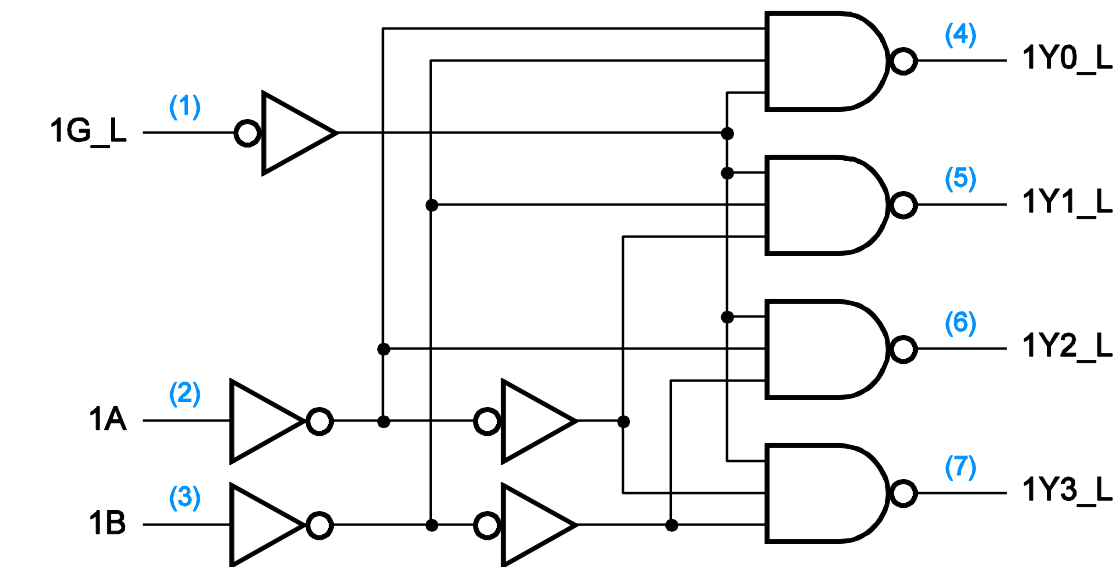Truth table for $\frac{1}{2}$ of the circuit 74x139 (dual 2-to-4 decoder) [Wakerly]. Input enable G_L is active low




(a)

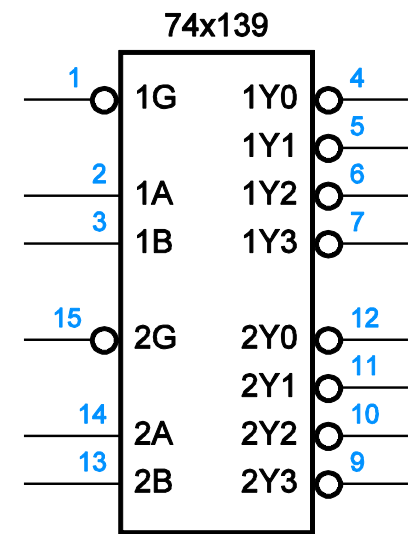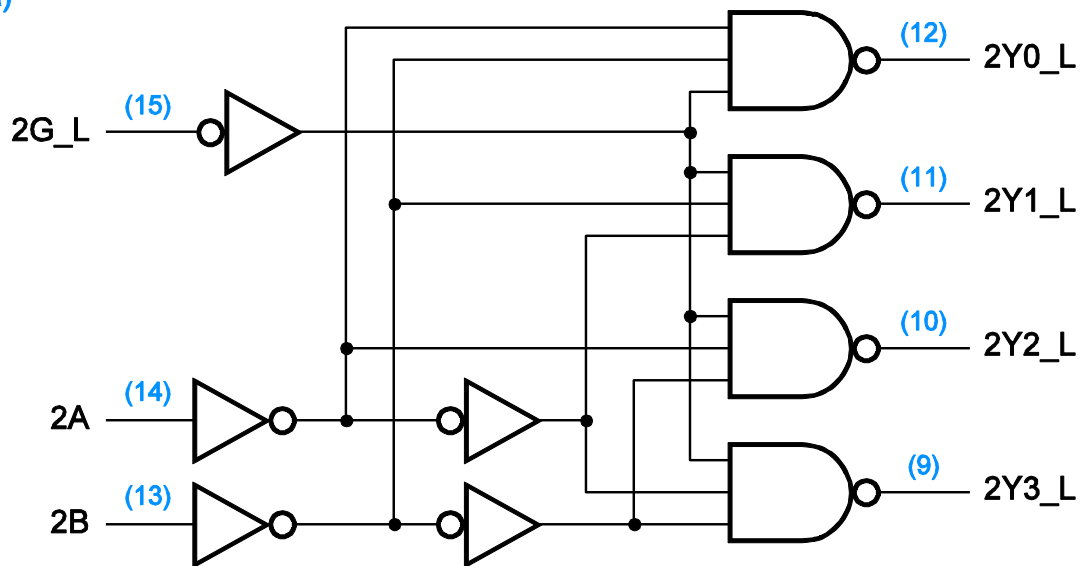

(b)

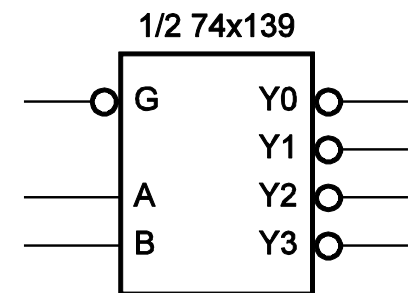Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e



(c)

Fig 6-34 [Wakerly]. 74x139 (a) logic diagram (b) inputs and outputs

74x138 3-to-8 decoder

Table 5-7 Truth table for a 74x138 3-to-8 decoder.

<i>Inputs</i>						<i>Outputs</i>							
G1	G2A_L	G2B_L	C	B	A	Y7_L	Y6_L	Y5_L	Y4_L	Y3_L	Y2_L	Y1_L	Y0_L
0	x	x	x	x	x	1	1	1	1	1	1	1	1
x	1	x	x	x	x	1	1	1	1	1	1	1	1
x	x	1	x	x	x	1	1	1	1	1	1	1	1
1	0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	0	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	0	0	1	1	1	0	1	1	1	1
1	0	0	1	0	1	1	1	0	1	1	1	1	1
1	0	0	1	1	0	1	0	1	1	1	1	1	1
1	0	0	1	1	1	0	1	1	1	1	1	1	1

Truth table for 74x138 decoder [Wakerly]

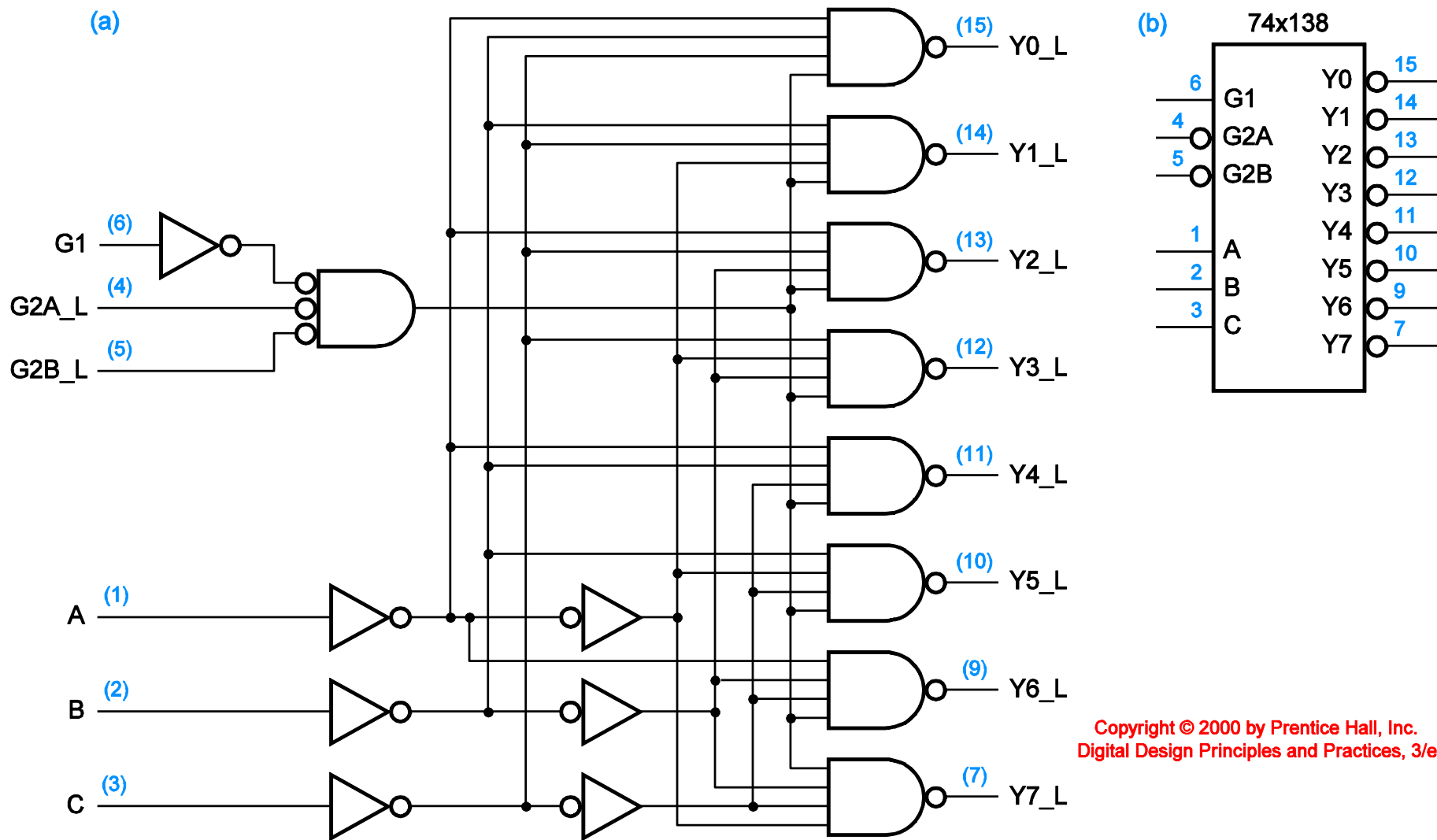


Fig 6-35 [Wakerly] Logic diagram for the 74x138 3-to-8 decoder

Implementation of logic functions with decoders

The decoders can be used to realize logic function, like in figure 9.15. The decoder implements the functions f_1 and f_2 :

$$f_1(a, b, c, d) = m_1 + m_2 + m_4$$

$$f_2(a, b, c, d) = m_4 + m_7 + m_9$$

Indeed, applying De Morgan, we have:

$$f_1 = (m'_1 m'_2 m'_4)'$$

$$f_2 = (m'_4 m'_7 m'_9)'$$

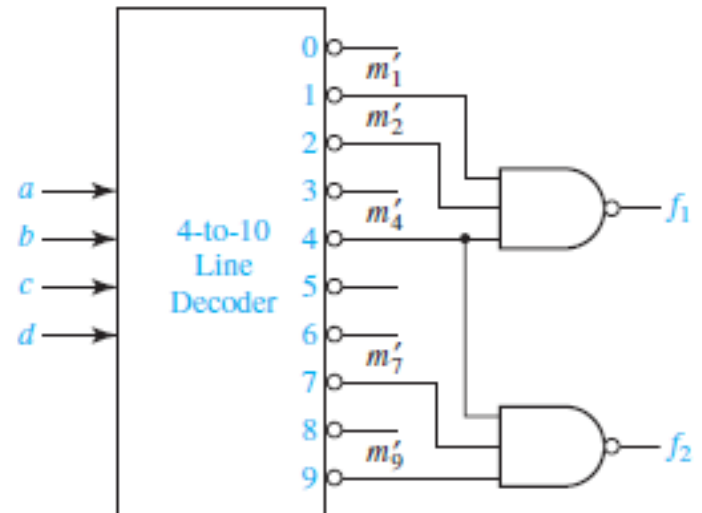


FIGURE 9-15
Realization of a
Multiple-Output
Circuit Using a
Decoder

Fig 9-15.
Implementing
logic functions
with decoders
[RothKinney]

Cascading decoders

Figure 6-38 [Wakerly]: Cascading two 3-to-8 decoders to obtain a 4-to-16 decoder:

The 3 less significant input lines N2, N1, N0 are connected to the data inputs of each decoder

The most significant input line N3 is used to select between the two decoder circuits:

N3 selects first decoder when it is low (0) => less significant input lines DEC0_L – DEC7_L active

If N3=1 second decoder selected, most significant output lines DEC8_L to DEC15_L active


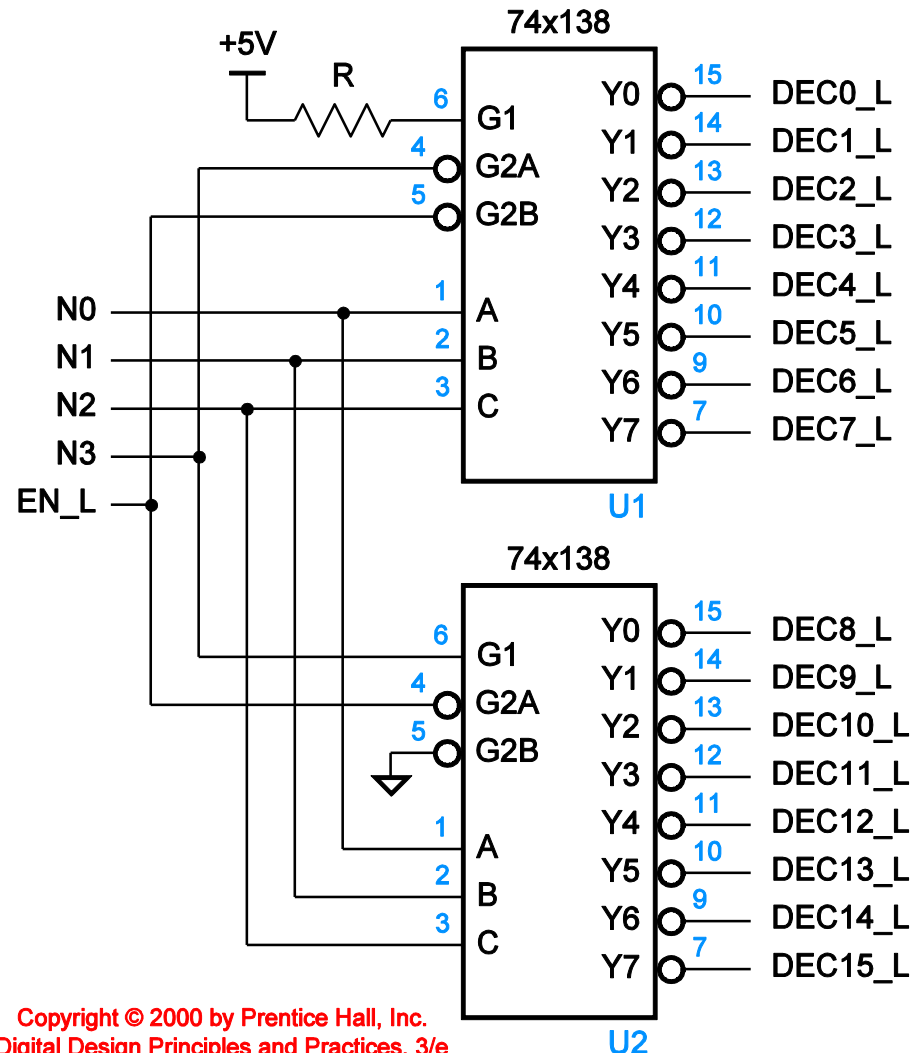


Fig 6-37 [Wakerly]:
designing a 5-to-32
decoder using 74x138
decoders

Most significant lines
N4, N3 are decoded by
a 2-to-4 decoder in
order to obtain selection
inputs for the 4 3-to-8
decoders that have lines
N2, N1, N0 as inputs

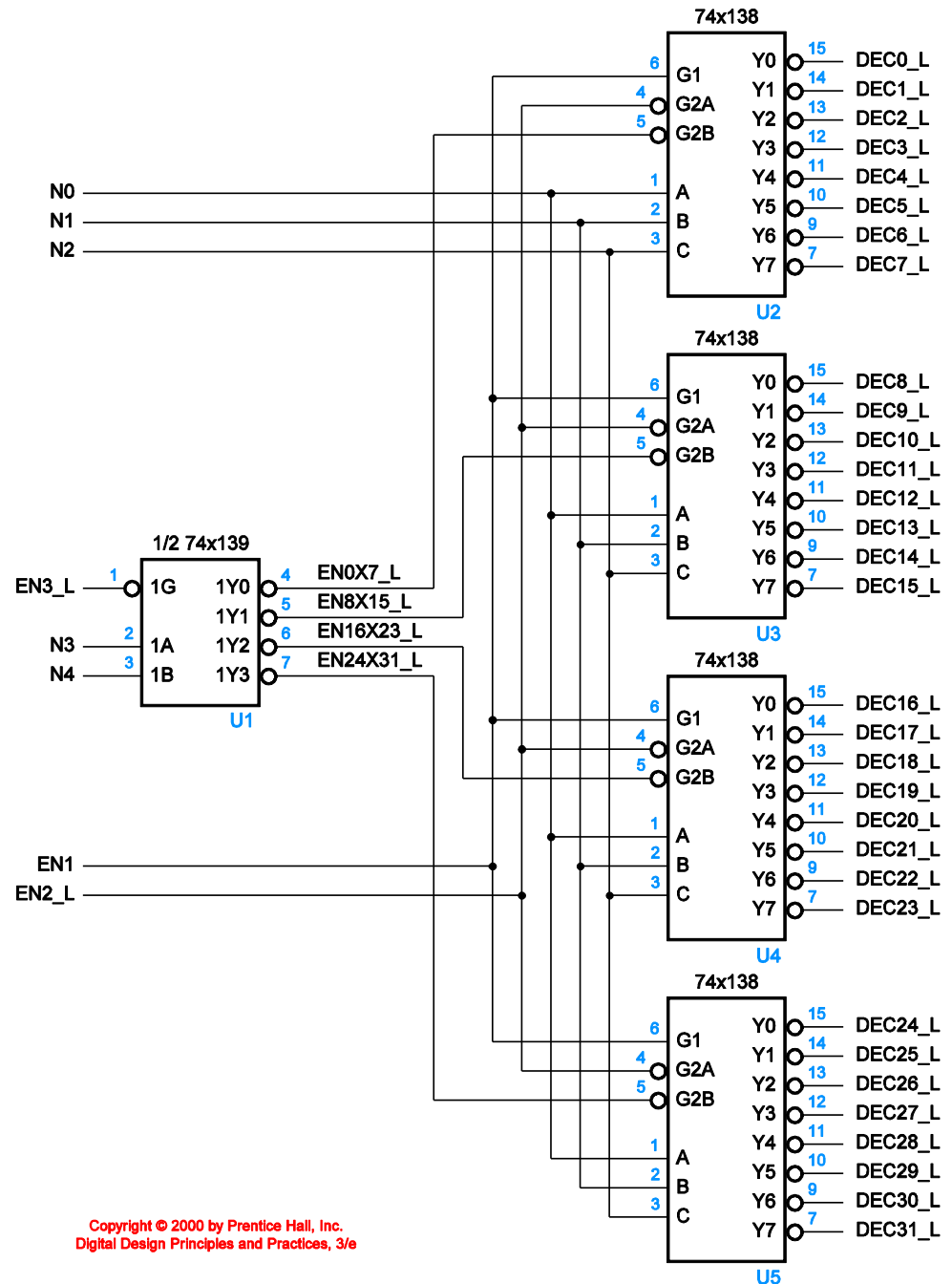First decoder can be
replaced with a 3-to-8
decoder, using only
inputs lines B for N4
and A for N3, with input
C connected to GND.



Encoders

- An encoder performs the inverse function of a decoder.
- Figure 9.16 shows an 8-to-3 priority encoder and its truth table.
- If only one input y_i is active (i.e. it is 1) and the other inputs are 0, then the abc outputs represent the binary number i .
- If more than one y_i are 1 at the same time, then the output will be defined using a priority scheme, e.g. the priority increases from y_0 to y_7 (highest input determine the output)
 - If y_7 is active, the others input do not care and so on.
 - Here X means don't care, not unknown value, the notation can be confusing !
- Output d is 1 if any input is 1 (active), otherwise it is 0.

Priority encoders

FIGURE 9-16
An 8-to-3 Priority
Encoder

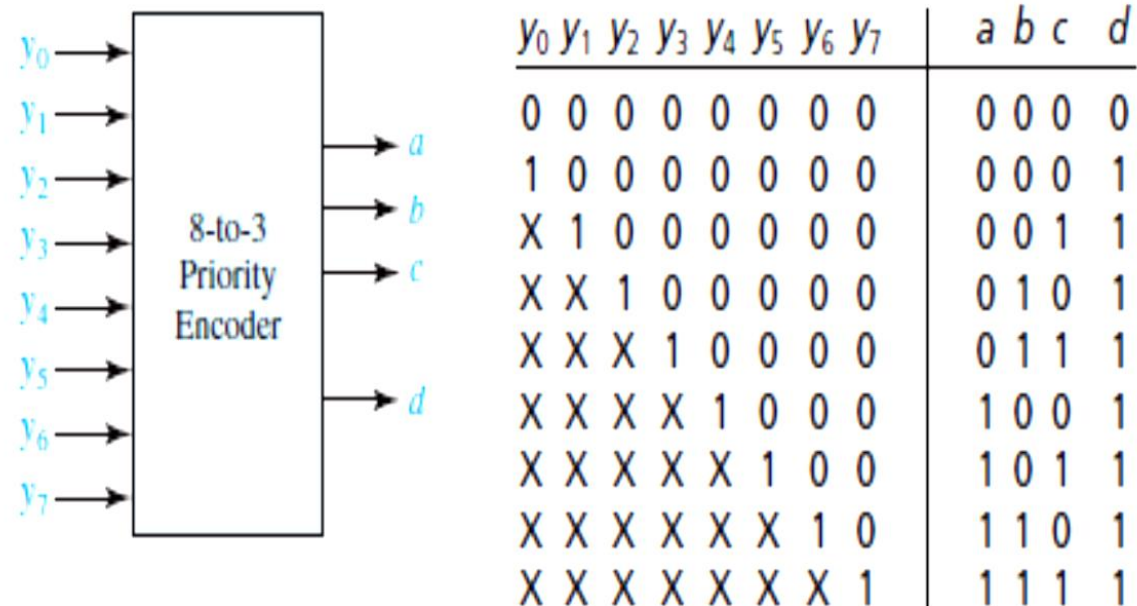


Fig 9.16. Priority encoder with truth table. [RothKinney]

Priority encoders

- A naïve implementation:
 - From the table from fig 9.16 it follows that:
 - $a = y_4 + y_5 + y_6 + y_7$
 - $b = y_2 + y_3 + y_6 + y_7$
 - $c = y_1 + y_3 + y_5 + y_7$
 - $d = y_0 + y_1 + y_2 + y_3 + y_4 + y_5 + y_6 + y_7$
 - But, if $y_2=1$ and $y_4=1$ in the same time, the output of the decoder will be $abc = 110$, which corresponds to y_6 !!!
 - The problem was that we did not prioritize between the inputs y_0, \dots, y_7 when more than one is active


Priority encoders

- The correct solution: we have to take into account the priorities of the inputs
- In this case, the priority increases from y_0 to y_7
- We define eight intermediate variables, H_0 to H_7 , such that H_i is 1 if and only if y_i is the highest priority 1 input [Wakerly]:
 - $H_7 = y_7$
 - $H_6 = y_6 \cdot y_7'$
 - $H_5 = y_5 \cdot y_6' \cdot y_7'$
 - ...
 - $H_0 = y_0 \cdot y_1' \cdot y_2' \cdot y_3' \cdot y_4' \cdot y_5' \cdot y_6' \cdot y_7'$

Priority encoders


- Now the equations for a, b, c and d become:
 - $a = H4 + H5 + H6 + H7$
 - $b = H2 + H3 + H6 + H7$
 - $c = H1 + H3 + H5 + H7$
 - $d = H0 + H1 + H2 + H3 + H4 + H5 + H6 + H7$

Priority encoders

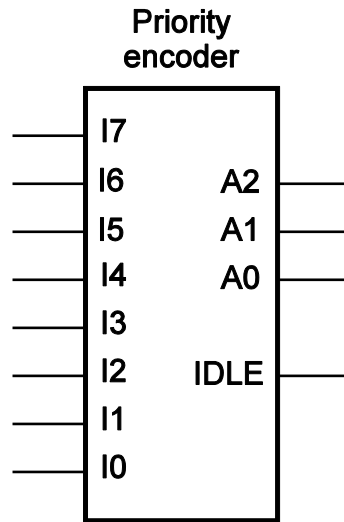

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Fig 6-47 [Wakerly]: Logic symbol for a generic 8-input priority encoder

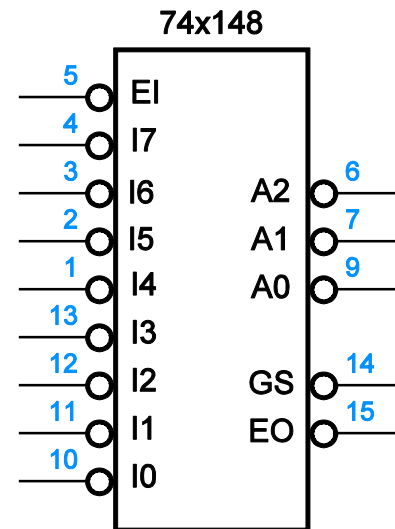

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Fig 6-48 [Wakerly]: Logic symbol for the 74x148 8-input priority encoder

Truth table for 74x148 priority encoder


Table 5-23 Truth table for a 74x148 8-input priority encoder.

<i>Inputs</i>									<i>Outputs</i>				
EI_L	I0_L	I1_L	I2_L	I3_L	I4_L	I5_L	I6_L	I7_L	A2_L	A1_L	A0_L	GS_L	EO_L
1	x	x	x	x	x	x	x	x	1	1	1	1	1
0	x	x	x	x	x	x	x	0	0	0	0	0	1
0	x	x	x	x	x	x	0	1	0	0	1	0	1
0	x	x	x	x	x	0	1	1	0	1	0	0	1
0	x	x	x	x	0	1	1	1	0	1	1	0	1
0	x	x	x	0	1	1	1	1	1	0	0	0	1
0	x	x	0	1	1	1	1	1	1	0	1	0	1
0	x	0	1	1	1	1	1	1	1	1	0	0	1
0	0	1	1	1	1	1	1	1	1	1	1	0	1
0	1	1	1	1	1	1	1	1	1	1	1	1	0

Table 6-27
[Wakerly]
Truth table
for 74x148

74x148 priority encoder

- The output line GS_L (group select, or “got something”) is active when at least one input is active
- Output EO (EO_L) is active when no input line is active
- EO is used for cascading priority encoders: it will be connected to the EI_L input of the next priority encoder (the less significant one)
- Next figure shows the main application of priority encoders: there are $N=2^n$ requestors and the outputs of the encoder indicates which requestor is active at any time

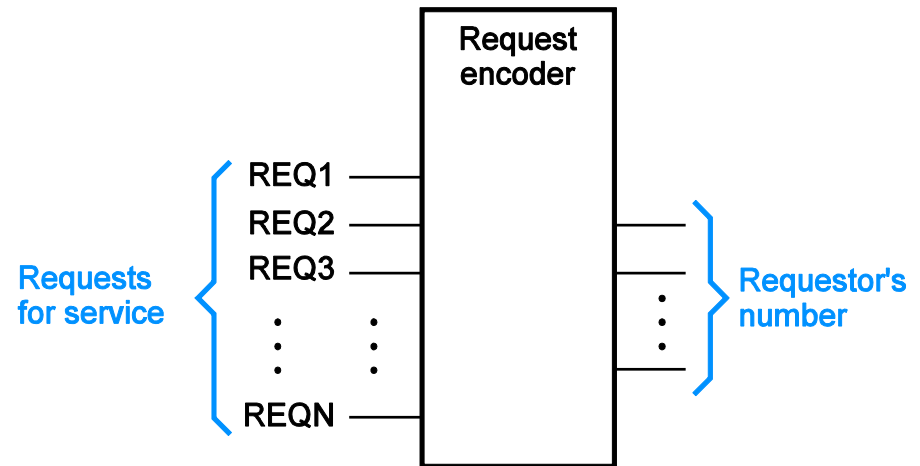

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Fig 6-45 [Wakerly]: A system with requestor and the request encoder

Commercial multiplexers.

Applications of multiplexers and demultiplexers


- Commercial multiplexers
- Expanding multiplexers
- Multiplexers, demultiplexers and busses
- Using Shannon expansion theorem for designing with multiplexers

Fig 6-60
[Wakerly]: The
74x151 8:1
multiplexer. (a)
logic diagram

(b) Logic symbol

The output
appears both
active-1 (Y) and
active-0 (Y_L)

EN_L: enable
input

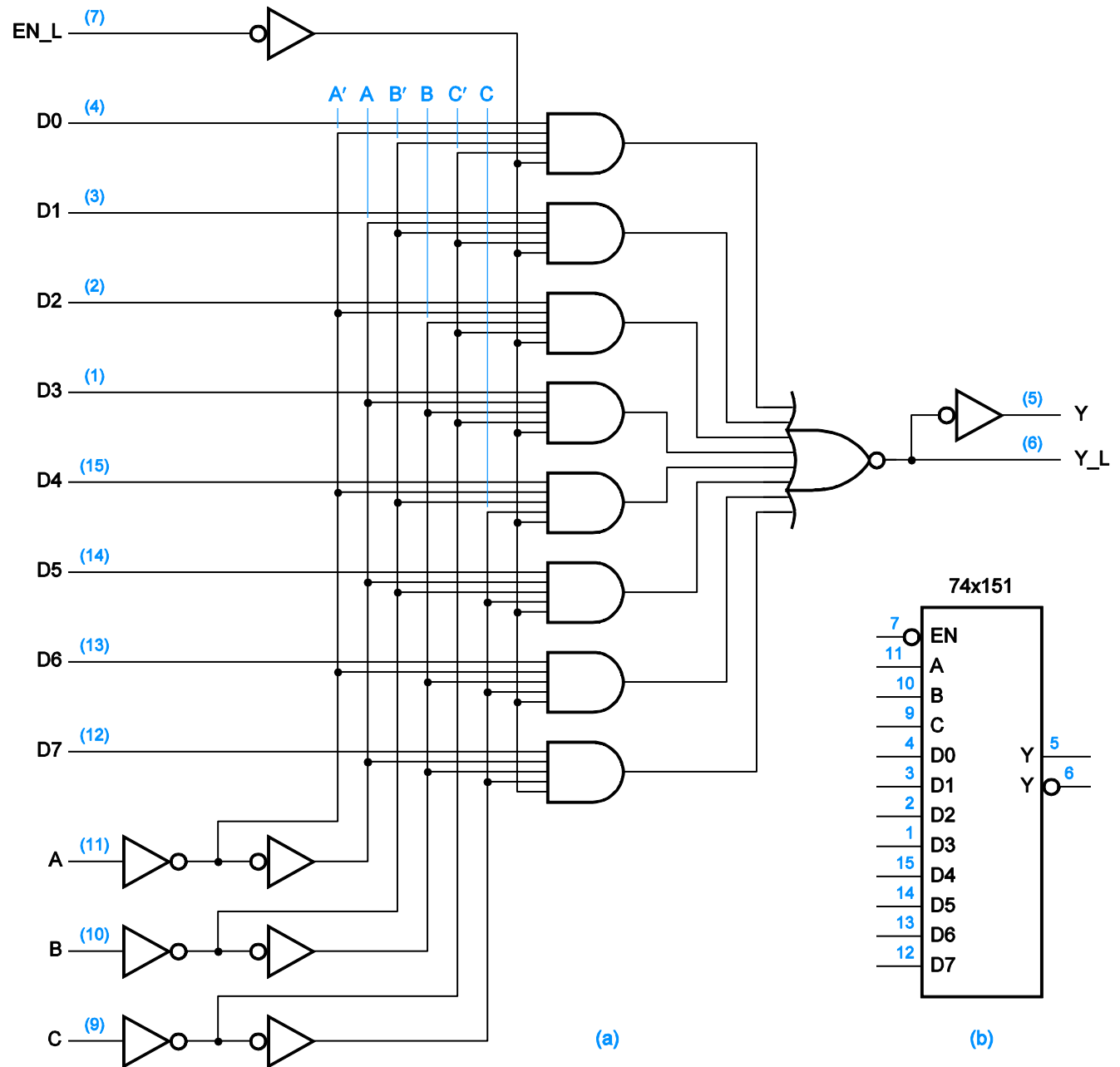

Truth table for 74x151 MUX

Table 5-34
Truth table for a
74x151 8-input,
1-bit multiplexer.

Table 5-34 [Wakerly]. Truth
table for 8-input, 1-bit
multiplexer

<i>Inputs</i>				<i>Outputs</i>	
EN_L	C	B	A	Y	Y_L
1	x	x	x	0	1
0	0	0	0	D0	D0'
0	0	0	1	D1	D1'
0	0	1	0	D2	D2'
0	0	1	1	D3	D3'
0	1	0	0	D4	D4'
0	1	0	1	D5	D5'
0	1	1	0	D6	D6'
0	1	1	1	D7	D7'

74x157 MUX



<i>Inputs</i>		<i>Outputs</i>			
G_L	S	1Y	2Y	3Y	4Y
1	x	0	0	0	0
0	0	1A	2A	3A	4A
0	1	1B	2B	3B	4B

Table 5-35
Truth table for a
74x157 2-input,
4-bit multiplexer.

Table 5-35 [Wakerly]: truth table for a 74x157 2-input, 4-bit MUX

Figure on next slide: Fig 6-64 from [Wakerly]: 74x157 2-input 4-bit multiplexer: (a) logic diagram; (b) logic symbol


74x151 contains 4 2:1 MUXes

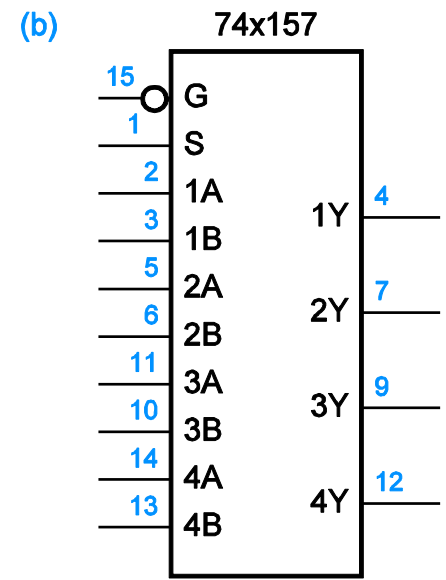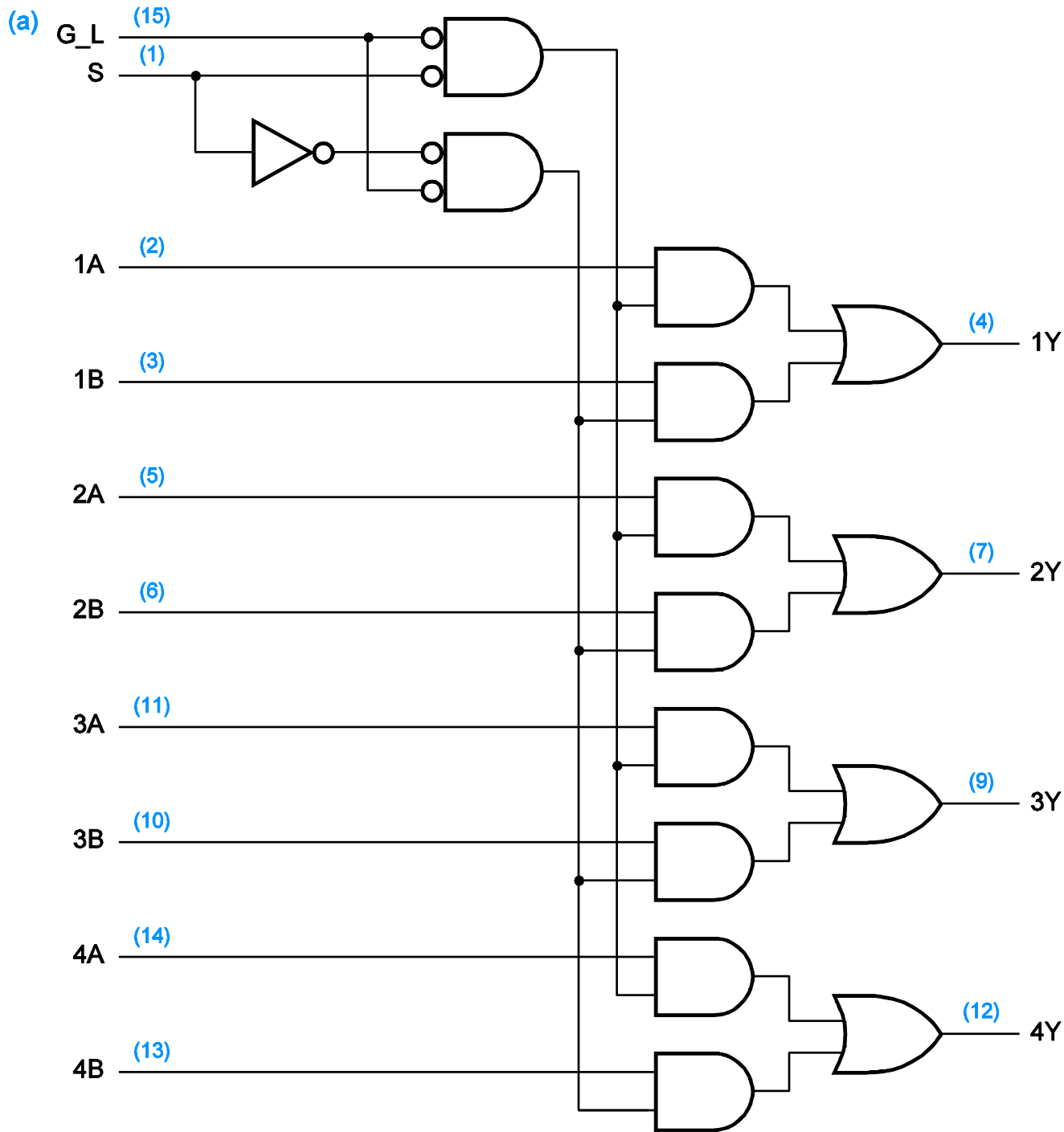

Expanding multiplexers

- If we want to make a larger MUX from the available MUXes and decoders
- In the next figure (figure 6-62 from [Wakerly]): Combining 74x151s to make a 32-to-1 multiplexer) 3 of the selection lines are common (XA0 to XA2), while the most significant selections line are inputs to the decoder
- The outputs of the decoder are connected to the enable inputs of the MUXes in order to select them
- The outputs of the 4 MUXes are connected by a NAND gate (from a 74x20 IC)

Fig 6-52
[Wakerly]:
combining
74x151s to
make a 32-to-1
multiplexer

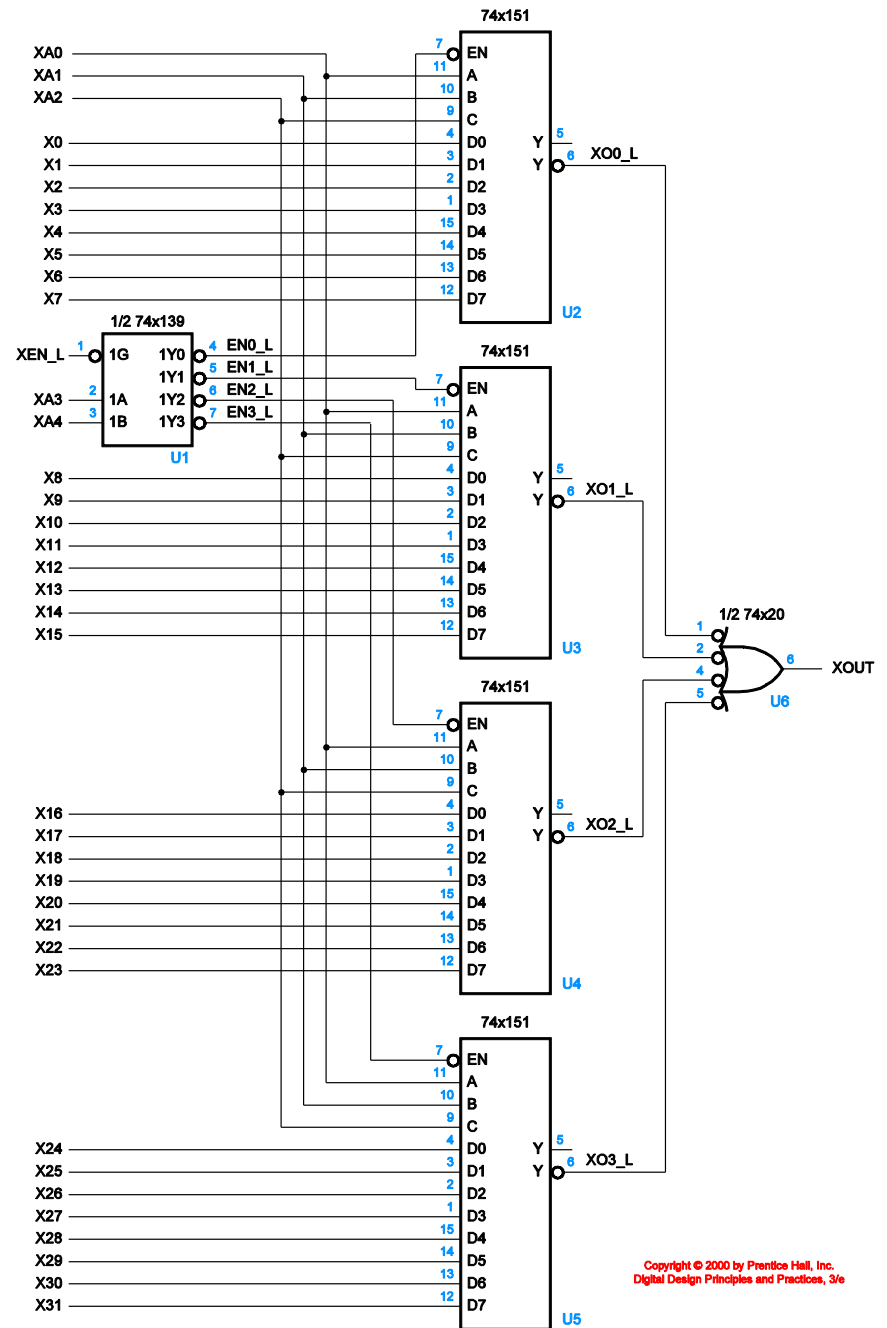


Multiplexers, demultiplexers and buses


- A demultiplexer (DEMUX) performs the opposite function of a multiplexer:
 - Has one data input
 - Has n selection inputs
 - And 2^n outputs
 - The input will be connected to the output whose number is given by the binary number that represents the selection inputs
- A MUX can be used to select 1-out-of- n sources of data and transmit it on a bus
- At the other end of the bus a DEMUX can be used to route the bus data to one of the destinations
- A demultiplexer can be implemented with a decoder (e.g. with a 74x139 2-to-4 decoder, or with a 74x138 3-to-8 decoder)

MUX-DEMUX

Figure 6-64
[Wakerly] A
mux driving a
bus and a
demultiplexer
receiving the
bus: (a)
switch
equivalent; (b)
symbols

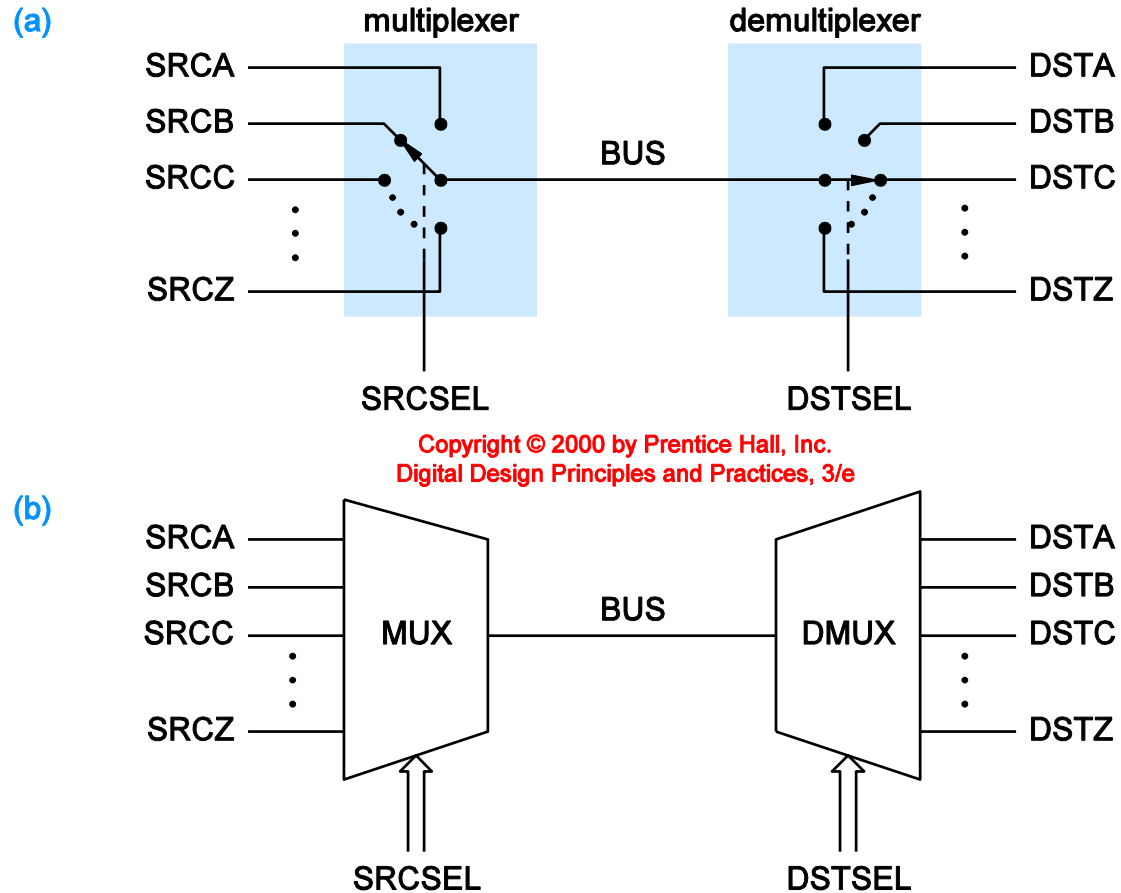

Demux implemented with a decoder

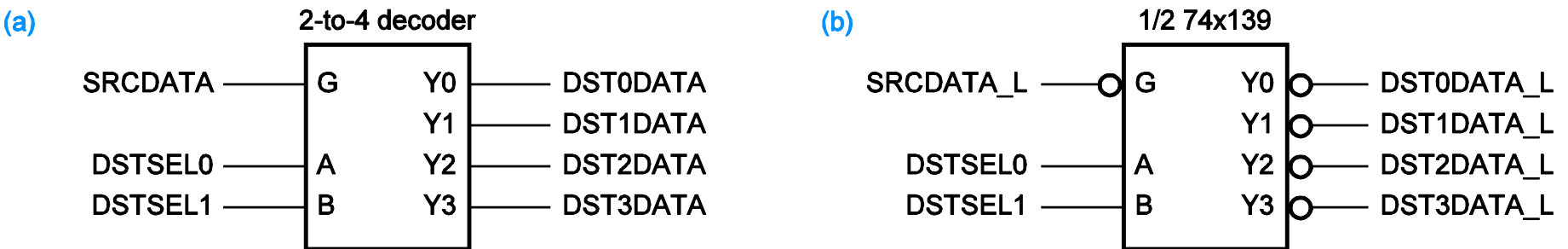

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Fig 5-67 [Wakerly], third edition: Using a 2-to-4 binary decoder as a 1-to-4 demultiplexer (a) generic decoder; (b) 74x139

The input data is connected to the enable input of the decoder; the selection inputs of the demux are connected to the selection inputs of the decoder.

Using Shannon expansion theorem for designing with multiplexers

- $$\begin{aligned} f(x_1, x_2, \dots, x_{i-1}, x_i, x_{i+1}, \dots, x_n) &= \\ &= x_i' \cdot f(x_1, x_2, \dots, x_{i-1}, 0, x_{i+1}, \dots, x_n) + \\ &+ x_i \cdot f(x_1, x_2, \dots, x_{i-1}, 1, x_{i+1}, \dots, x_n) = \\ &= x_i' \cdot f_0 + x_i \cdot f_1 \end{aligned}$$

This means that we can implement an n-variable function with an (n-1) variable function and a 2:1 mux

In general, we can implement (realize) any n-variable function ($n > 4$) with $2^{(n-4)}$ 4-bit function generators and one $2^{(n-4)}$ -to-1 mux.

This is very useful in FPGAs, where the internal structure contains many MUXes and 4-bit function generators (FGs)


Example of expansion theorem

- Example for a 6-variable function
$$G(a,b,c,d,e,f)=a' \cdot G(0,b,c,d,e,f) + a \cdot G(1,b,c,d,e,f) = a' \cdot G_0 + a \cdot G_1;$$
- $G_0 = b' G(0,0,c,d,e,f) + b \cdot G(0,1,c,d,e,f) = b' \cdot G_{00} + b \cdot G_{01}$
- $G_1 = b' G(1,0,c,d,e,f) + b \cdot G(1,1,c,d,e,f) = b' G_{10} + b \cdot G_{11}$
- An implementation is shown in the next figure

Designing with MUXes

Fig 9-36 [RothKinney]:
Realization of 5- and
6-variable function with
function generators
(FGs) and MUXes.

 
In fig 9-36 (b) the 4:1
MUX is implemented
as a tree of 2:1 MUXes



Read-Only Memories

- A read-only memory (ROM) is an array of semiconductor devices that are interconnected to store an array of binary data
- Once stored in the ROM, the binary data can be read, but cannot be modified (under normal operating conditions)
- *A ROM implements (i.e. stores) the truth table of a function (or of several functions)*
- Figure 9.17 shows a ROM with 3 input lines and 4 output lines
- Each output pattern stored in the ROM is called a *word*
- Since the ROM has 3 input lines, it means that it can store $2^3=8$ words.

FIGURE 9-17
An 8-Word \times 4-Bit
ROM

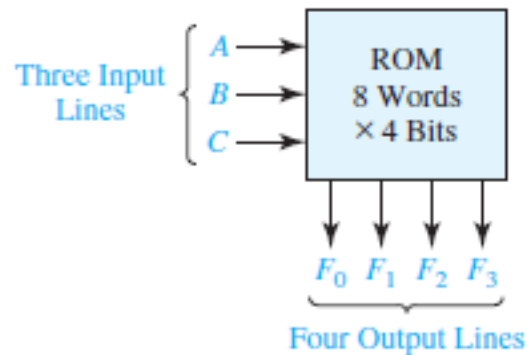

(a) Block diagram

A	B	C	F_0	F_1	F_2	F_3
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1


Typical Data
Stored in
ROM
(2^3 words of
4 bits each)

(b) Truth table for ROM

Fig 9-17. [RothKinney] A 8-word x 4 bit ROM

- In general a ROM with n input lines and m output lines can store 2^n words, each word having m bits. (fig 9.18)
- One input lines combination serve as an address to select one of the 2^n words:
 - When the input combination is applied to the inputs, the outputs will contain the word stored at that address
 - In fig 9-18, when 00...11 is applied to the input (the address lines) of the ROM, the output will be 110...010
- A $2^n \times m$ ROM can realize m functions of n variables
- Typical sizes of ROMs: from 32 words x 4bits to 512 K words x 8 bits and even 1024 K words x 8 bits (1 Mega word of 8 bits)
- For memories 1 K = $2^{10} = 1024$!! (10 address lines)
- With 20 address lines we can address $2^{20} = 1024 \times 1024 = 1$ Mega words of data

FIGURE 9-18
Read-Only Memory
with n Inputs and
 m Outputs

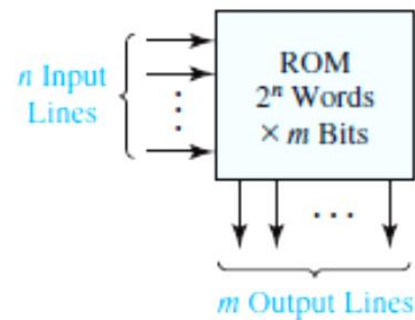

n Input Variables	m Output Variables
00 ... 00	100 ... 110
00 ... 01	010 ... 111
00 ... 10	101 ... 101
00 ... 11	110 ... 010
...	...
11 ... 00	001 ... 011
11 ... 01	110 ... 110
11 ... 10	011 ... 000
11 ... 11	111 ... 101

Typical Data Array Stored in ROM (2^n words of m bits each)

Fig 9-18. [RothKinney] ROM with n inputs and m outputs

Basic ROM structure

A ROM consists of a decoder and a memory array (see fig 9-19)

When a pattern of 0s and 1s is applied to the decoder inputs, exactly one of the decoder's outputs will be active.

The active output line of the decoder will select a word from the memory array.

The selected word will appear at the outputs of the ROM.

FIGURE 9-19
Basic ROM
Structure

 


Fig 9-19 [RothKinney]
Basic ROM structure

ROM example 1


- Figure 9-20 shows a possible internal structure of the ROM from fig 9-17.
- The decoder generates the 8 minterms that can be obtained with 3 input variables
- The memory array forms the four output functions F_0 , F_1 , F_2 , F_3 by ORing together selected minterms.
 - F_0 is the sum of minterms 0,1,4 and 6
 - F_1 is the sum of minterms 2,3,4,6 and 7, etc
- A switching element is placed at the intersection of a word line and an output line if the corresponding minterm has to be included in the output function
 - If the minterm will not be included in the output function the switching element remains unconnected (it will be omitted)
- If the minterm is 1, then the word line is 1 and the output line connected to it will be also 1

Example 1

- If none of the word lines connected to an output line is 1, then the pull-down resistors will cause the output to be 0
- In this way the switching elements form an OR array: an OR gate for each of the output lines
- The minterms that form a function are connected to the output line that corresponds to that function.

Example 1

FIGURE 9-20
An 8-Word \times 4-Bit
ROM

 

Example 1

The functions implemented by the ROM from figure 9-20 are given aside.

What is important is the minterm list representation of the functions, not their minimized form.

Figure 9-21 gives the equivalent OR gate for function F_0

Bellow we have the algebraic minimization of F_0 :

$$F_0 = A' \cdot B' \cdot C' + A' \cdot B' \cdot C + A \cdot B' \cdot C' + A \cdot B \cdot C' = A' \cdot B' \cdot (C + C') + A \cdot C' \cdot (B + B') = A' \cdot B' + A \cdot C'$$

$$F_0 = \sum m(0, 1, 4, 6) = A' B' + A C'$$


$$F_1 = \sum m(2, 3, 4, 6, 7) = B + A C'$$

$$F_2 = \sum m(0, 1, 2, 6) = A' B' + B C'$$

$$F_3 = \sum m(2, 3, 5, 6, 7) = A C + B$$

Functions implemented by the ROM from fig 9-20.

FIGURE 9-21
Equivalent OR Gate
for F_0

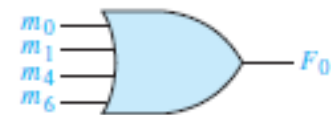


Another example: code converter

- Figure 9-22 shows the truth table and the logic circuit for a code converter that converts a 4-bit binary number to the ASCII representation of its hexadecimal digit
- ASCII: American Standard Code for Information Interchange: a 7-bits code for representing digits, letters and other characters.
 - The character A is represented by the combination 41_{16} , or 100 0001 in binary, etc
- From the table we can see that $A_5=A_4$ and $A_6=A_4'$ => the ROM will have 4 input lines and 5 output lines (16 words by 5 bits)
- The switching elements at the intersections of rows and columns are marked by X's:
 - An X indicates that the switching element is presented and connected
 - No X means that the corresponding element is absent or not connected

Code converter


FIGURE 9-22
Hexadecimal-to-
ASCII Code
Converter

Input				Hex Digit	ASCII Code for Hex Digit						
W	X	Y	Z		A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
0	0	0	0	0	0	1	1	0	0	0	0
0	0	0	1	1	0	1	1	0	0	0	1
0	0	1	0	2	0	1	1	0	0	1	0
0	0	1	1	3	0	1	1	0	0	1	1
0	1	0	0	4	0	1	1	0	1	0	0
0	1	0	1	5	0	1	1	0	1	0	1
0	1	1	0	6	0	1	1	0	1	1	0
0	1	1	1	7	0	1	1	0	1	1	1
1	0	0	0	8	0	1	1	1	0	0	0
1	0	0	1	9	0	1	1	1	0	0	1
1	0	1	0	A	1	0	0	0	0	0	1
1	0	1	1	B	1	0	0	0	0	1	0
1	1	0	0	C	1	0	0	0	0	1	1
1	1	0	1	D	1	0	0	0	1	0	0
1	1	1	0	E	1	0	0	0	1	0	1
1	1	1	1	F	1	0	0	0	1	1	0

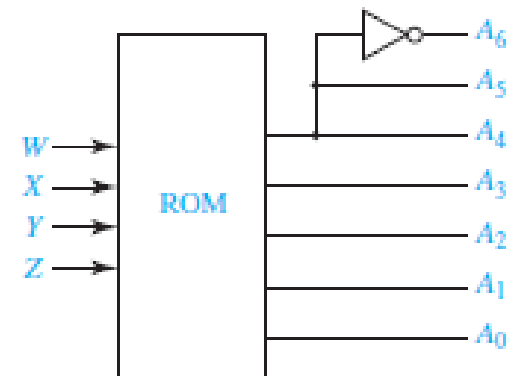

Code converter

FIGURE 9-23
ROM Realization of
Code Converter

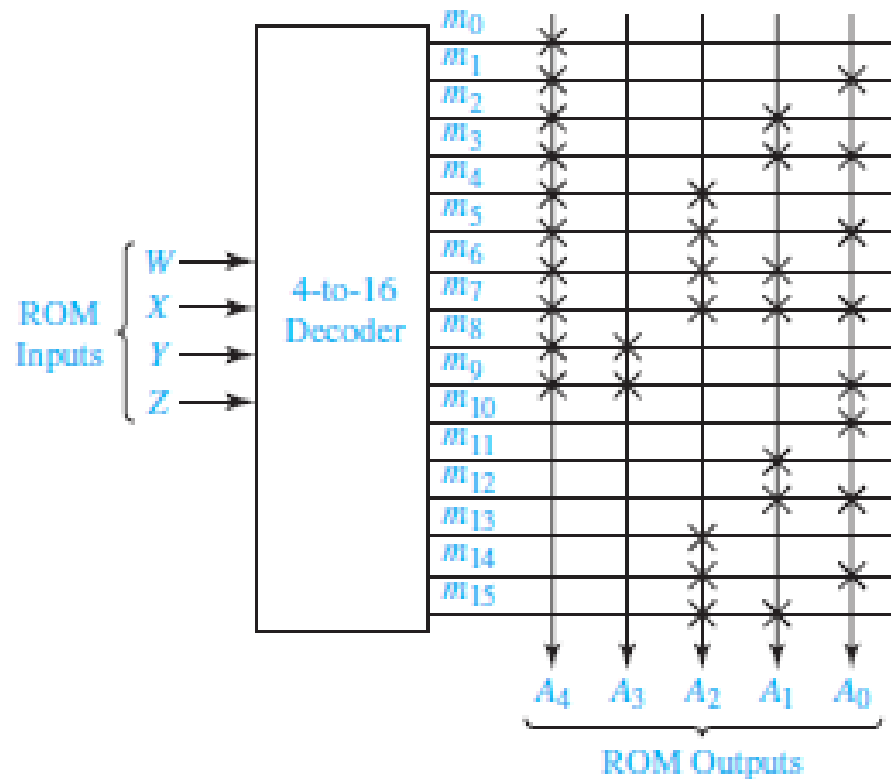

Types of ROMs

- The most common types of ROMs are:
 - Mask-programmable ROMs
 - Programmable ROMs (PROMs)
 - Electrically erasable ROMs
- Mask programmable ROMs:
 - They are programmed at the time of manufacture
 - Data is permanently stored and cannot be changed
 - The presence or omission of the switching elements is realized with a mask
 - The realization of a mask is expensive =>
 - This type of ROM is economically feasible only for a large quantity
- PROMs: can be programmed by the user, but only once

EEPROMs

- Can be erased and re-programmed
- They use a special charge-storage mechanism to enable or disable the switching elements in the memory array
- They are programmed with a PROM programmer
- Data stored is permanent, until erase
- The erasing and reprogramming cycles are limited (100-1000 times)
- Programming voltages are higher than in normal operation
- Also, programming times are much higher than their normal delays)
- Flash memories are similar to EEPROMs, but they use a different charge-storage mechanism
 - Also, have built-in programming and erase capabilities => don't need a special programmer

Programmable Logic Devices

- Types of Programmable Logic Devices (PLDs):
 - Programmable Logic Arrays (PLA)
 - Programmable Array Logic (PAL)
 - Complex Programmable Logic Devices (CPLD)
 - Field Programmable Gate Arrays (FPGA)
- CPLDs and FPGAs contain also sequential elements
 - They are used as target circuits for high-level synthesis: a description in a HDL like VHDL or Verilog is synthesized on a CPLD or FPGA.

PLA

- A PLA with n inputs and m outputs can realize m functions of n variables (like a ROM !)
- The internal organization of a PLA is different from that of a ROM (see fig 9-24):
 - The decoder is replaced by an AND array which realizes selected product terms of the input variables
 - The OR array ORs together the product terms in order to form the output functions
- A PLA implements a sum-of-products expression, while a ROM implements a truth table.
- The expressions implemented in a PLA are not necessarily minterms, as they are for ROMs, but rather minimized sum-of-products
- When the number of input variables is large, but the number of product terms is not very large, a PLA is more economical than a ROM.

PLA structure

FIGURE 9-24
Programmable
Logic Array
Structure

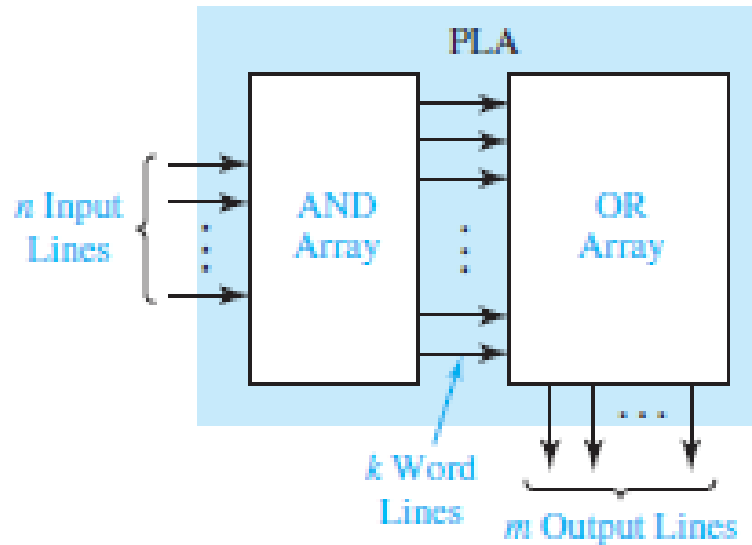



Fig 9-24 [RothKinney]: PLA structure.

PLA example 1

- PLA from fig 9-25 implements the same logic functions like the ROM from fig 9-20.
- While at ROM we used directly minterms, for PLA we use the *minimized functions*.
- Product terms are formed in the AND array by connecting switching elements at the appropriate points in the array.
 - For example, to form $A' \cdot B'$, switching elements connect the first word line with the A' and B' lines
- In the OR array, switching elements are connected to select the product terms needed for the output functions
 - For example, for $F_0 = A' \cdot B' + A \cdot C'$, switching elements connect $A' \cdot B'$ and $A \cdot C'$ lines with F_0 line.
- PLA connections are equivalent with AND-OR array from fig 9-26.

Example 1 PLA

FIGURE 9-25
PLA with Three
Inputs, Five Product
Terms, and Four
Outputs

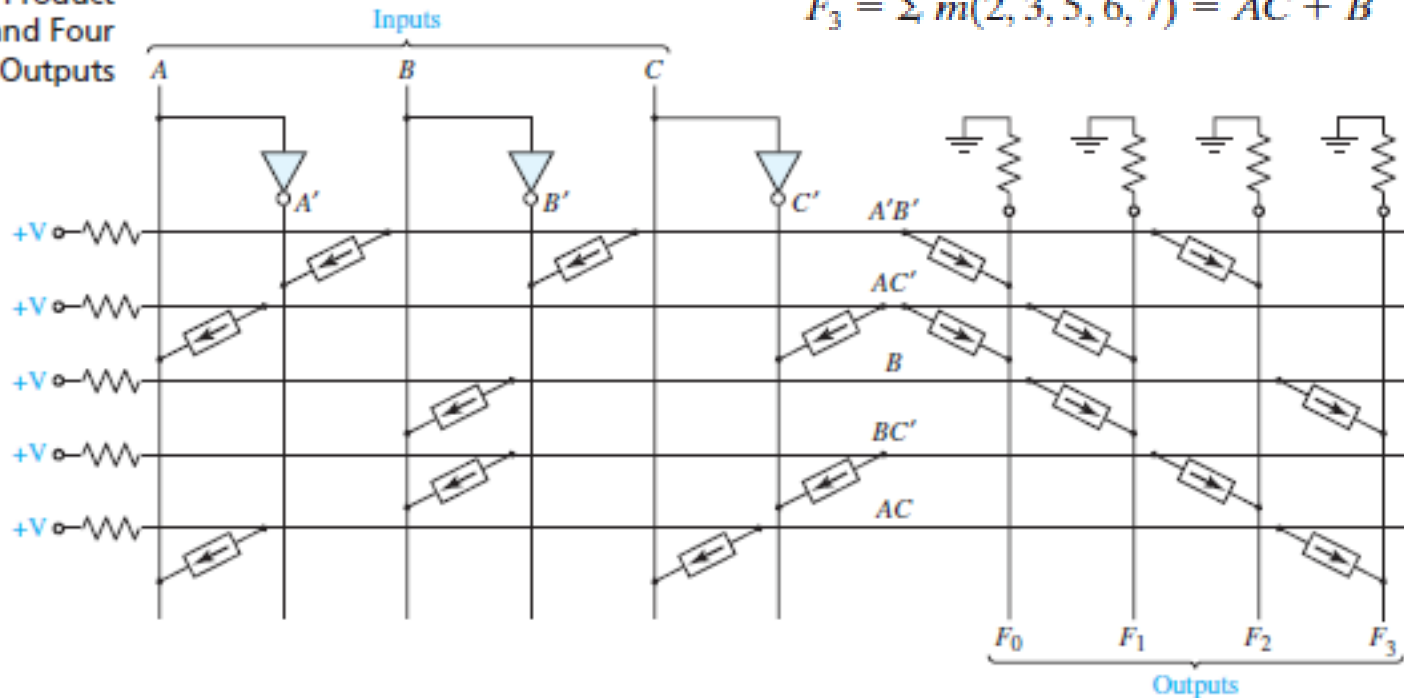

$$F_0 = \sum m(0, 1, 4, 6) = A'B' + AC'$$

$$F_1 = \sum m(2, 3, 4, 6, 7) = B + AC'$$

$$F_2 = \sum m(0, 1, 2, 6) = A'B' + BC'$$

$$F_3 = \sum m(2, 3, 5, 6, 7) = AC + B$$

Fig 9-25 [RothKinney]: PLA with three inputs, five product terms, and four outputs

Example 1 PLA

FIGURE 9-26
AND-OR Array
Equivalent to
Figure 9-25

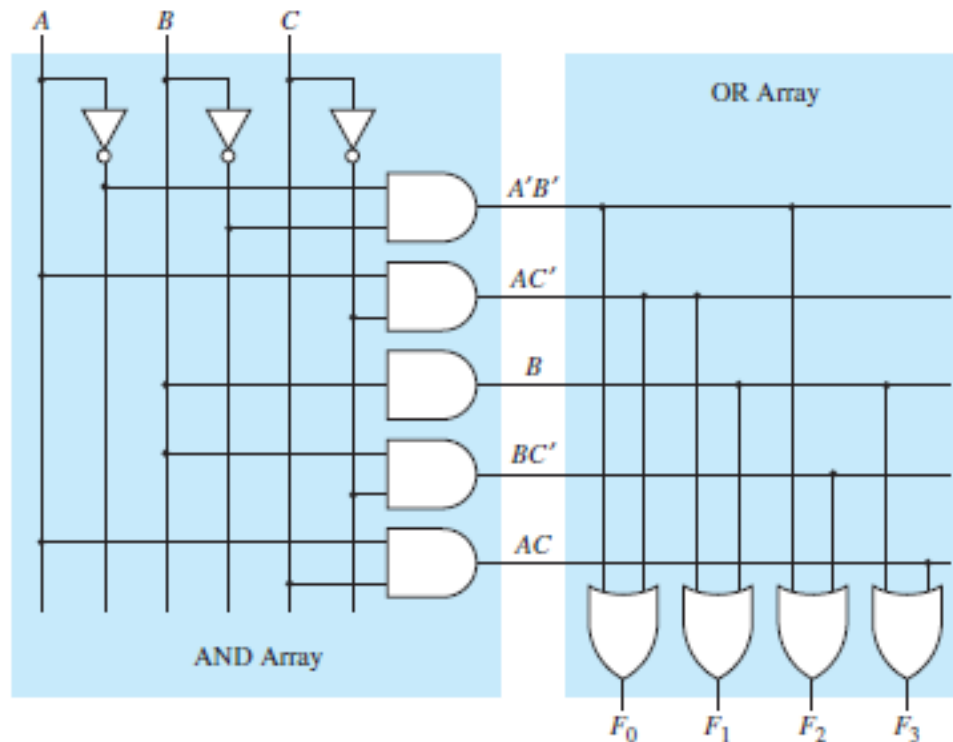


Fig 9-26 [RothKinney]: AND-OR array equivalent to Figure 9-25.

Example 1 PLA

Table 9-1
[RothKinney]:
PLA table for
Figure 9-25.

TABLE 9-1
PLA Table for
Figure 9-25

Product Term	Inputs A B C	Outputs F ₀ F ₁ F ₂ F ₃	
$A'B'$	0 0 –	1 0 1 0	$F_0 = A'B' + AC'$
AC'	1 – 0	1 1 0 0	$F_1 = AC' + B$
B	– 1 –	0 1 0 1	$F_2 = A'B' + BC'$
BC'	– 1 0	0 0 1 0	$F_3 = B + AC$
AC	1 – 1	0 0 0 1	

The content of a PLA can be specified by a PLA table.

The inputs indicate the product terms: symbols 0, 1 and – indicate if a variable is complemented, un-complemented, or not present in the corresponding product term.

The outputs indicate which product terms appears in the output functions: 1 indicate that the product term is present in the output function, 0 that it is not present.

Example 2


- In example 2 we implement equations (7-23b) from [RothKinney], shown below:
 - $f_1 = a' \cdot b \cdot d + a \cdot b \cdot d + a \cdot b' \cdot c' + b' \cdot c$
 - $f_2 = c + a' \cdot b \cdot d$
 - $f_3 = b \cdot c + a \cdot b' \cdot c' + a \cdot b \cdot d$
- The PLA table is in fig 9-27 (a).
- The PLA structure is given in Fig 9-27 (b).
- A dot at the intersection of a word line and an input or output line indicates the presence of a switching element in the array

FIGURE 9-27
PLA Realization of
Equations (7-23b)

a	b	c	d	f_1	f_2	f_3
0	1	–	1	1	1	0
1	1	–	1	1	0	1
1	0	0	–	1	0	1
–	0	1	–	1	0	0
–	–	1	–	0	1	0
–	1	1	–	0	0	1

(a) PLA table

Fig 9-27
[RothKinney]

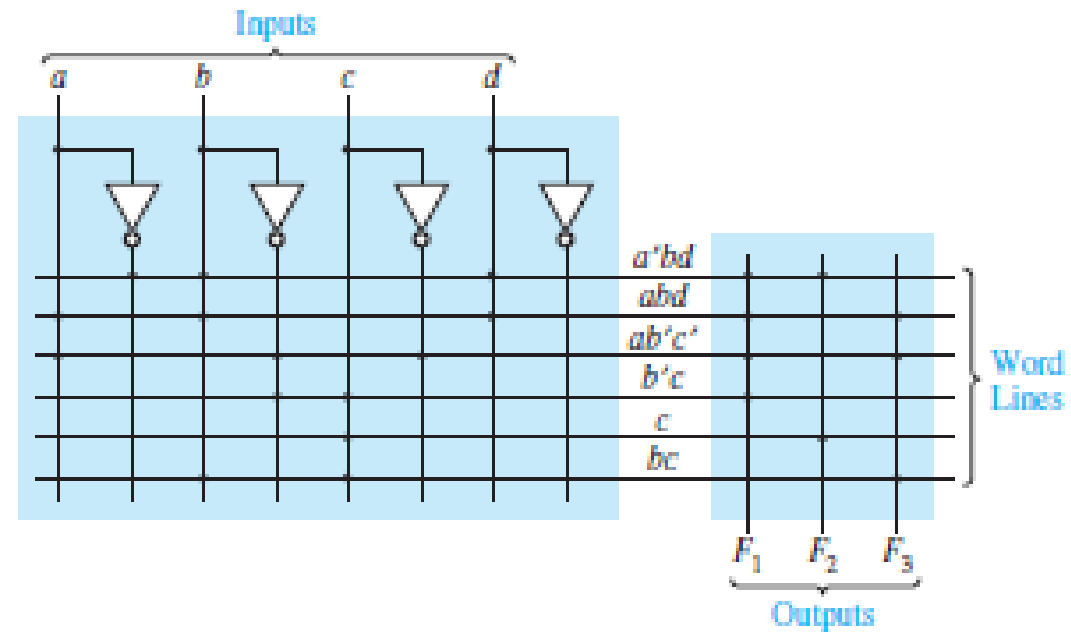

(b) PLA structure

PAL

Programmable Array Logic (PALs) are special cases of PLAs in which the AND array is programmable and the OR array is fixed.


The PALs are less expensive than PLAs.

Their functions are minimized independently of each other, since the AND terms cannot be shared between several OR gates.

Fig 9-28 shows a PLA segment (a) unprogrammed and (b) programmed.



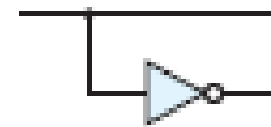The symbol from above represents an input buffer which is logically equivalent to:



Connections to the AND gate in a PAL are represented by X's, as shown [RothKinney]:



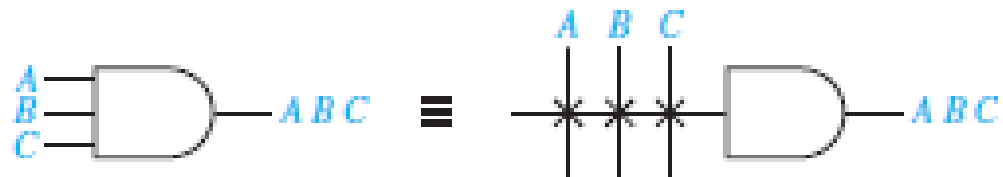


FIGURE 9-28
PAL Segment

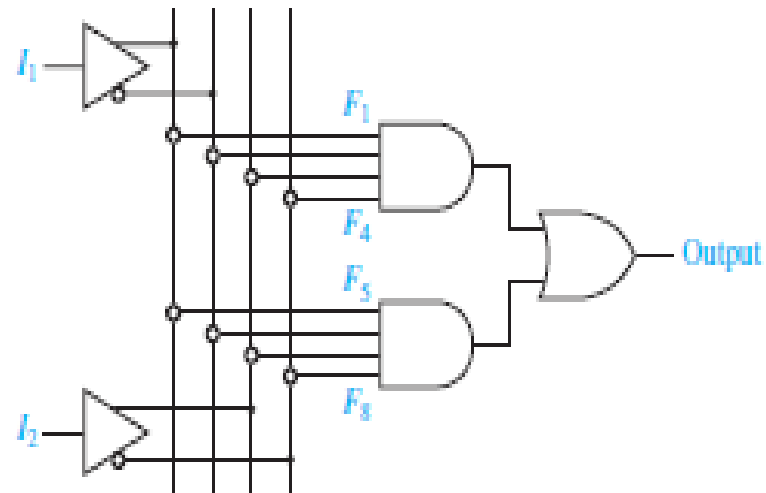

(a) Unprogrammed

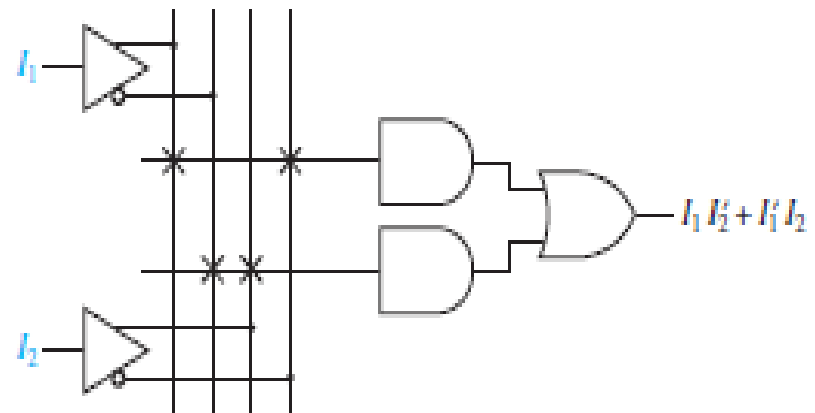

(b) Programmed

Fig 9-28
[RothKinney]:
PAL segment.

FIGURE 9-29
Implementation of
a Full Adder Using
a PAL

 


Fig 9-29
[RothKinney]:
Implementation of
a full-adder using
a PAL.

Equations of the
full adder are
given on the right
side:

$$\begin{aligned} \text{Sum} &= X'Y'C_{in} + X'YC'_{in} + XY'C'_{in} + XYC_{in} \\ C_{out} &= XC_{in} + YC_{in} + XY \end{aligned}$$

Exclusive-or Gates

The output of a exclusive-OR (XOR) gate is 1 only when only one of its inputs is 1, and 0 otherwise

XNOR gate produces the negated function of an XOR gate


XNOR function it is also called coincidence because it is 1 when the inputs are equal

X	Y	$X \oplus Y$ (XOR)	$(X \oplus Y)'$ (XNOR)
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

Table 5-45
Truth table for XOR
and XNOR functions.

Truth table for XOR and XNOR functions
[Wakerly]

Exclusive-OR gates

 

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e


Fig 6-69 [Wakerly]: Equivalent symbols for (a) XOR; (b) XNOR

The most common are the leftmost symbols

Exclusive-OR gates


Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Figure 6-68
[Wakerly]:
Multigate
designs for the
2-input XOR
function: (a)
AND-OR; (b)
three-level
NAND

 

Parity circuits

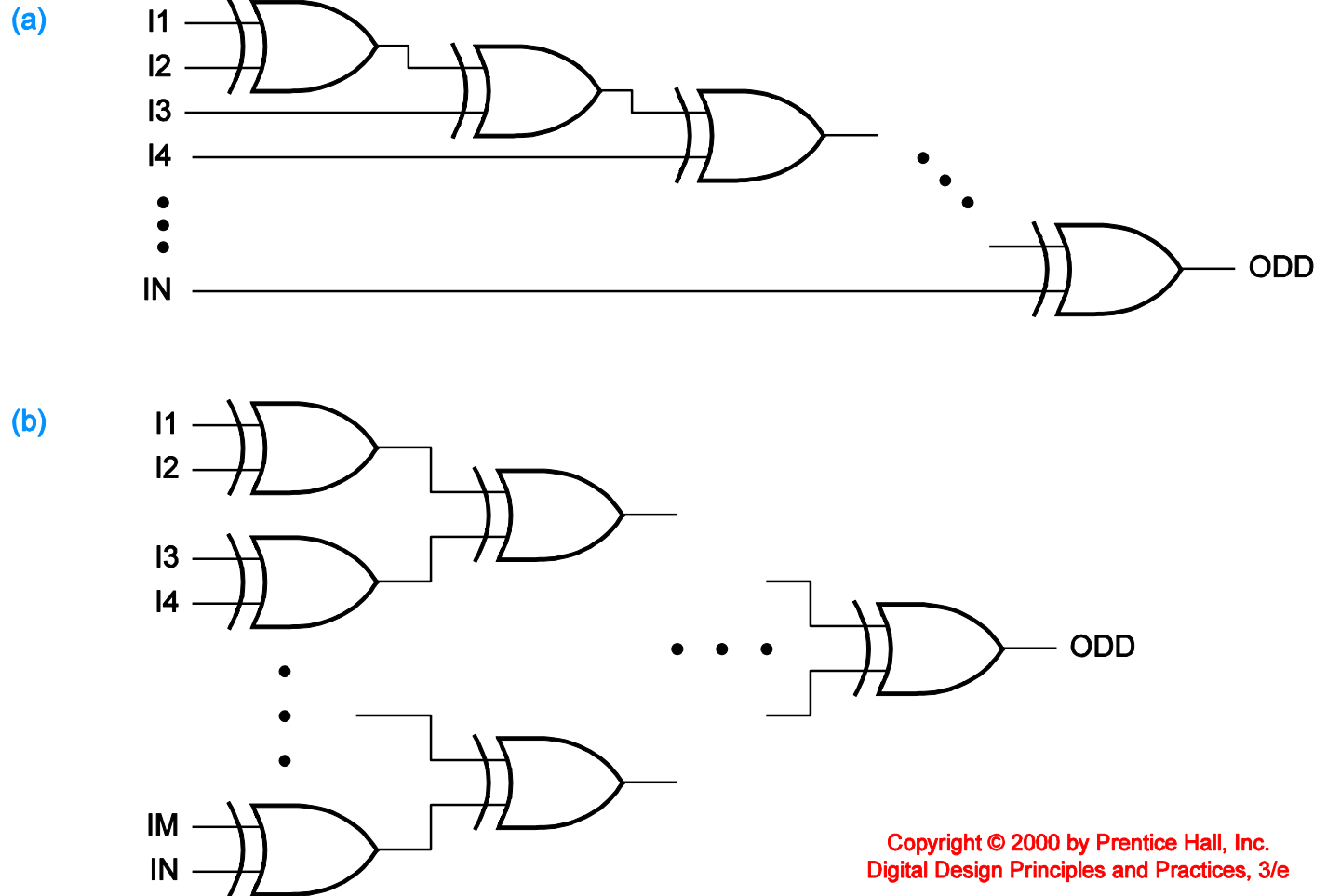XOR gates can be used in parity circuits, for determining the odd - parity of a number of bits: the output will be odd if the number of 1 bits is odd



Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Fig 6-70 [Wakerly]: Cascading XOR gates: (a) daisy-chain (b) tree structure

Active levels

Table 5-1
[Wakerly]:
different naming
conventions. We
have used the
convention from
the last line of the
table.

At circuits, active
low inputs and
outputs are
represented with
an inverting
bubble.

Table 5-1
Each line shows a
different naming
convention for active
levels.

<i>Active Low</i>	<i>Active High</i>
READY–	READY+
ERROR.L	ERROR.H
ADDR15(L)	ADDR15(H)
RESET*	RESET
ENABLE~	ENABLE
~GO	GO
/RECEIVE	RECEIVE
TRANSMIT_L	TRANSMIT

Active levels are the level on which signals are
“doing their things” [Wakerly].